

# Driver Amplifier for 7–Tesla MRI Smart Power Amplifier

presented by  
**Kevin Kolpatzeck**


supervised by  
**Prof. Dr.-Ing. Klaus Solbach**

Institute of Microwave and RF Technology

University of Duisburg Essen

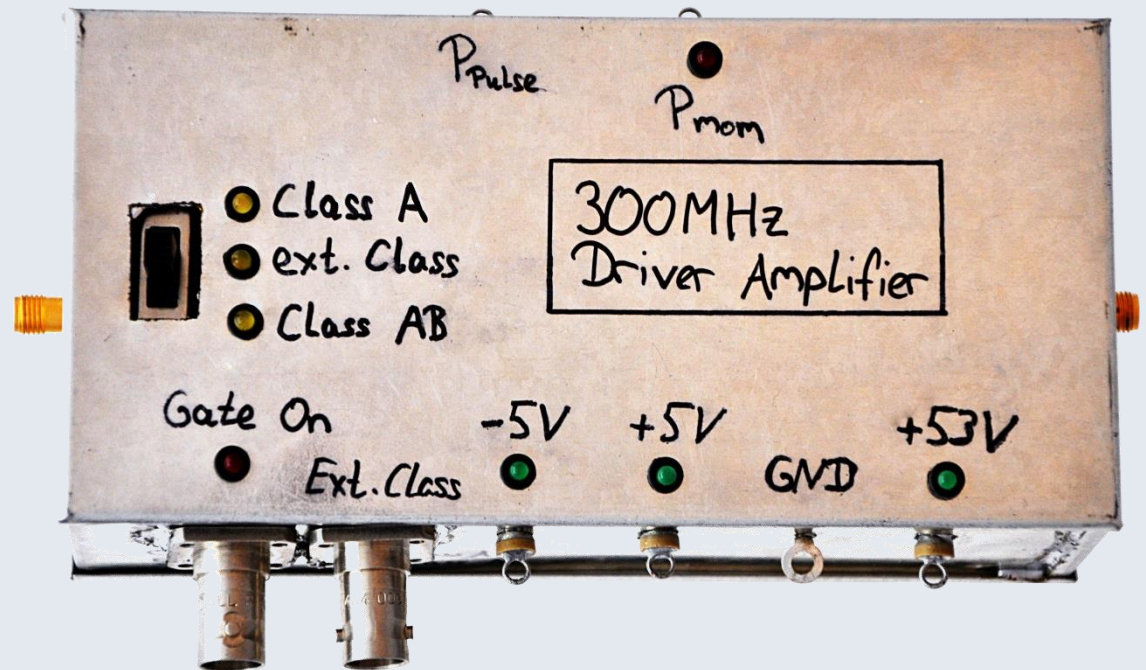
# Contents

- Introduction
- Concept
- Power Amplifier
- Gate Bias Circuit
- Voltage Regulator
- Power Monitor
- Assembly
- Conclusion



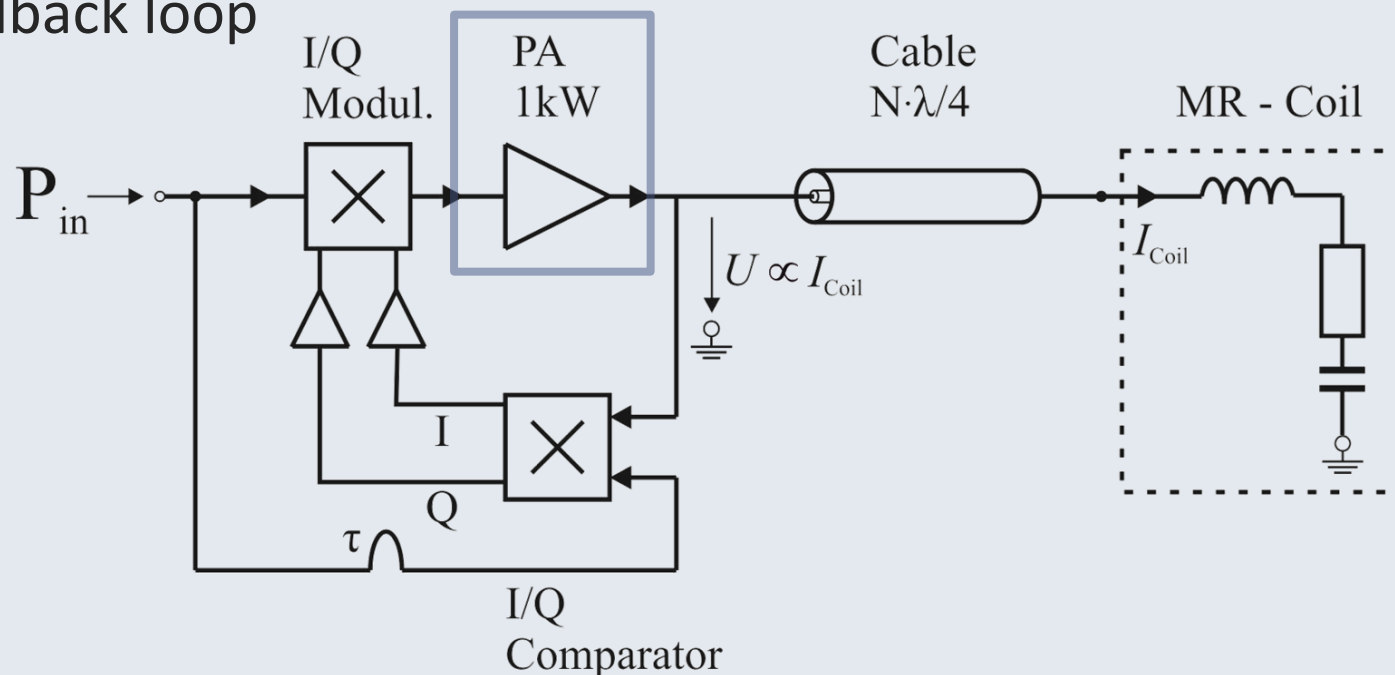
# Introduction

- 7 – Tesla MRI system employs 32 channels, each of which can produce 1 kW of pulsed power at 300 MHz
- each channel consists of an RF power amplifier and a cartesian feedback loop




# Introduction

- 1 kW – power amplifier:

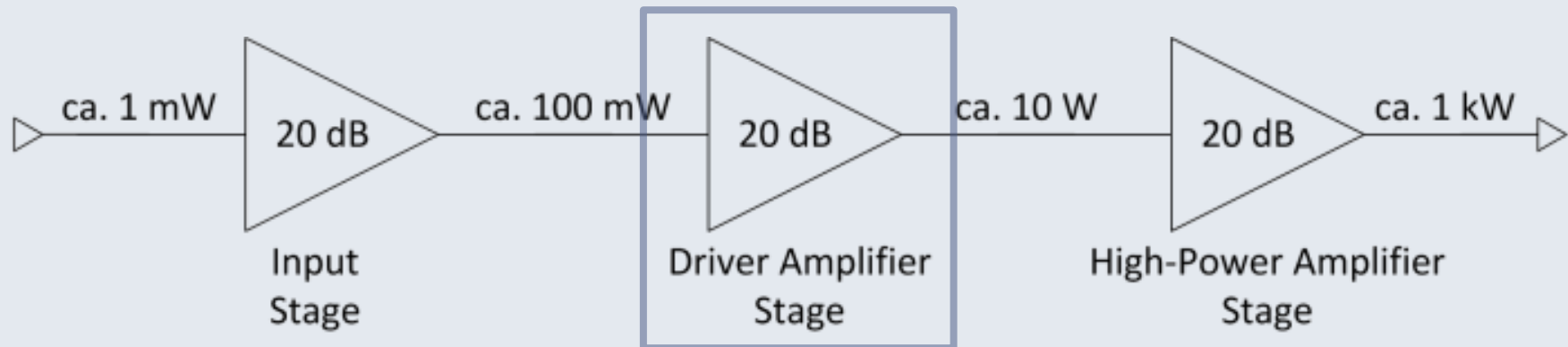

- Driver Amplifier will be used to evaluate some concepts for the driver and high-power stage, e.g.
  - Temperature Compensation
  - Power Monitor

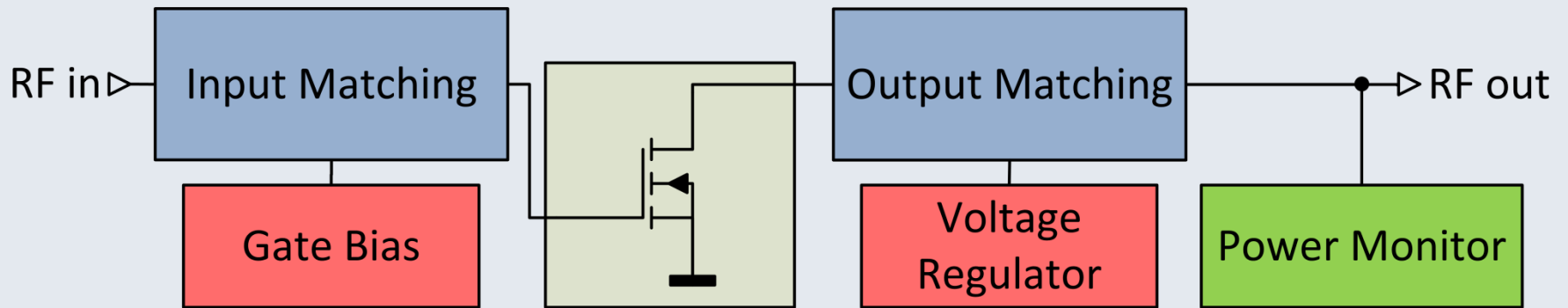- Driver Amplifier can be divided into five sub – circuits:



- Operating Point Stabilization
- Class A / Class AB Switching
- Temperature Compensation
- On / Off Switching


- Drain – Source Voltage Stabilization
- Load Regulation

- Easy & precise monitoring of
  - pulse power
  - momentary power

# Power Amplifier
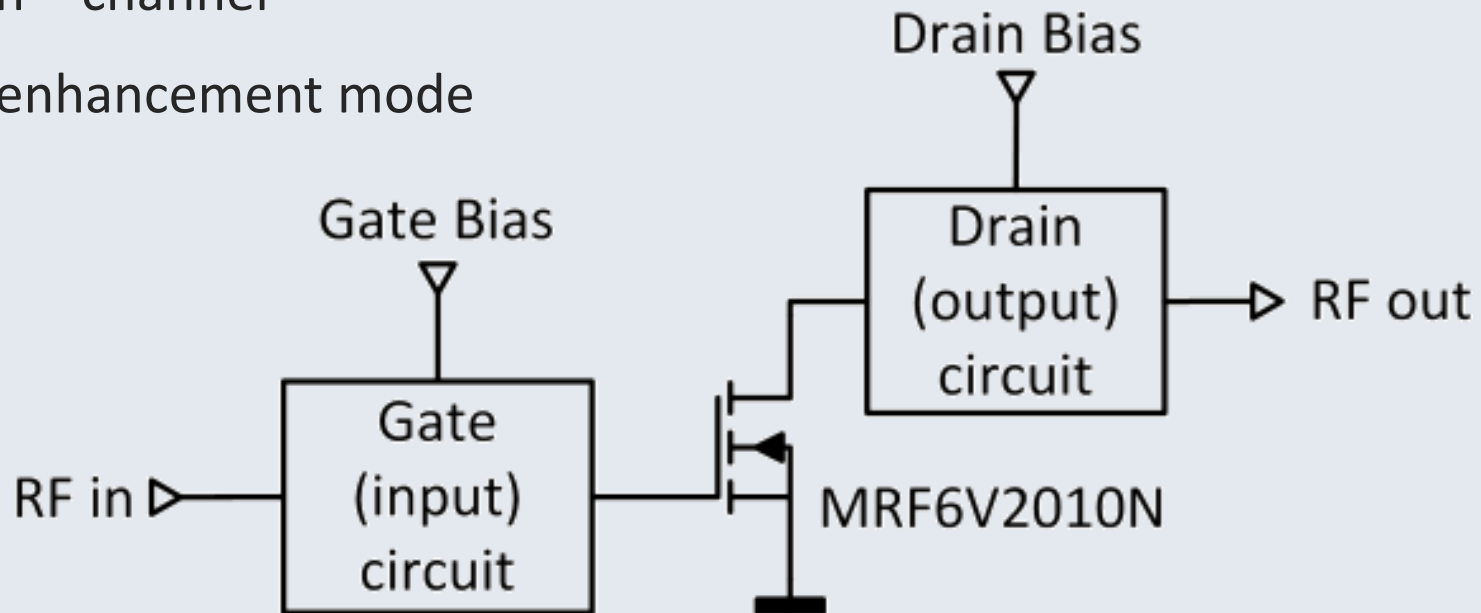
## Power Amplifier Concept


- Power amplifier is built around a Freescale MRF6V2010N
  - RF power MOSFET
  - n – channel
  - enhancement mode



# Power Amplifier
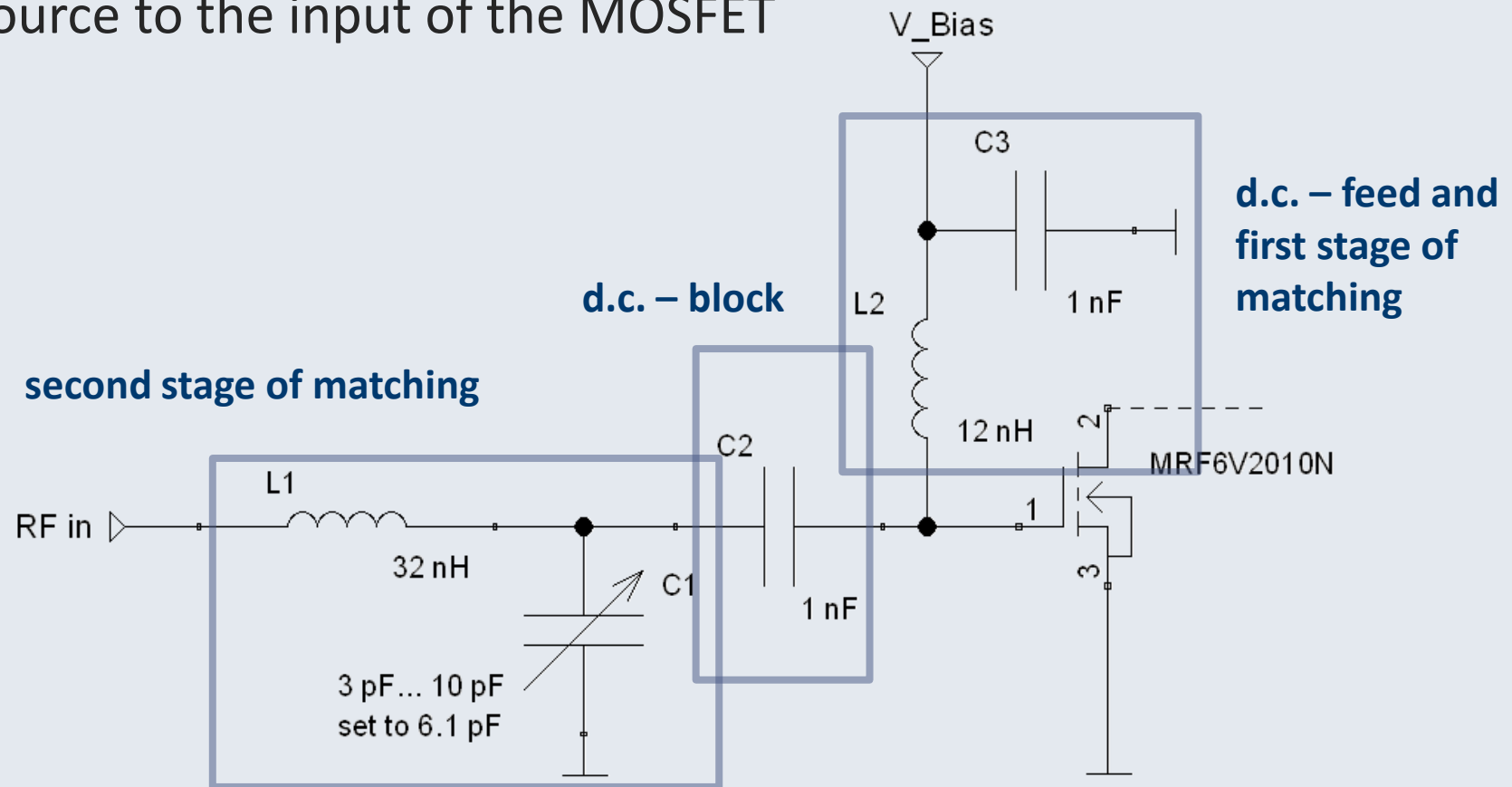
## Input Circuit


- Input circuit provides d.c. – feed and matching of the  $50 \Omega$  – source to the input of the MOSFET



# Power Amplifier
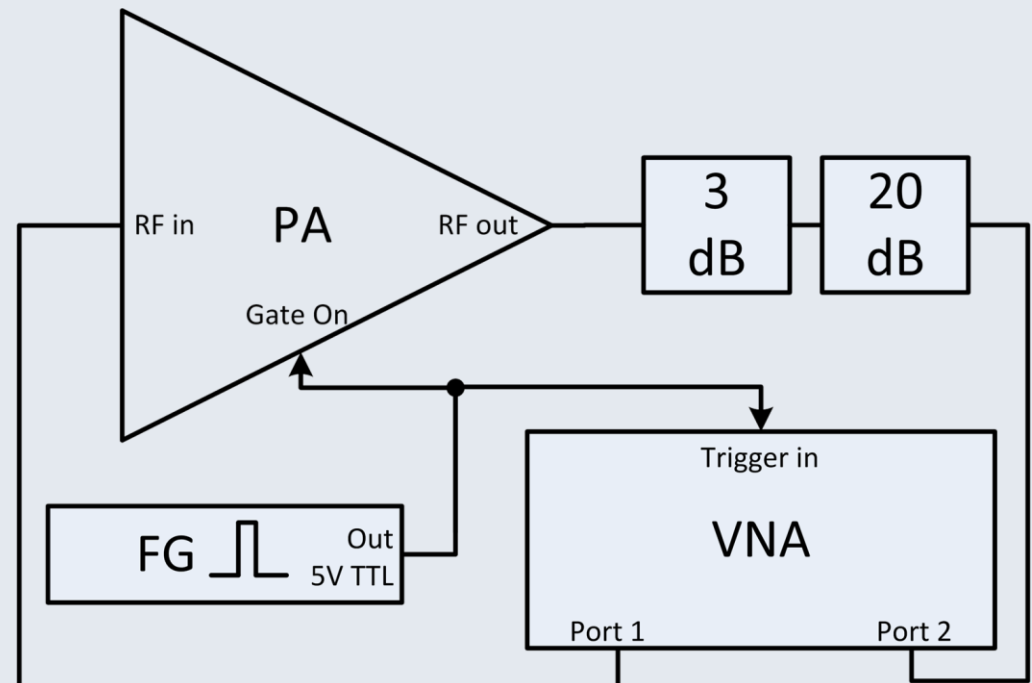
## Input Reflection Coefficient $S_{11}$

- Best match has been achieved with the two-stage matching network, that is however quite different from the manufacturer's recommendation
- Input reflection coefficient  $S_{11}$  has been measured with a vector network analyzer (VNA) for a Class A and a Class AB operating point






# Power Amplifier
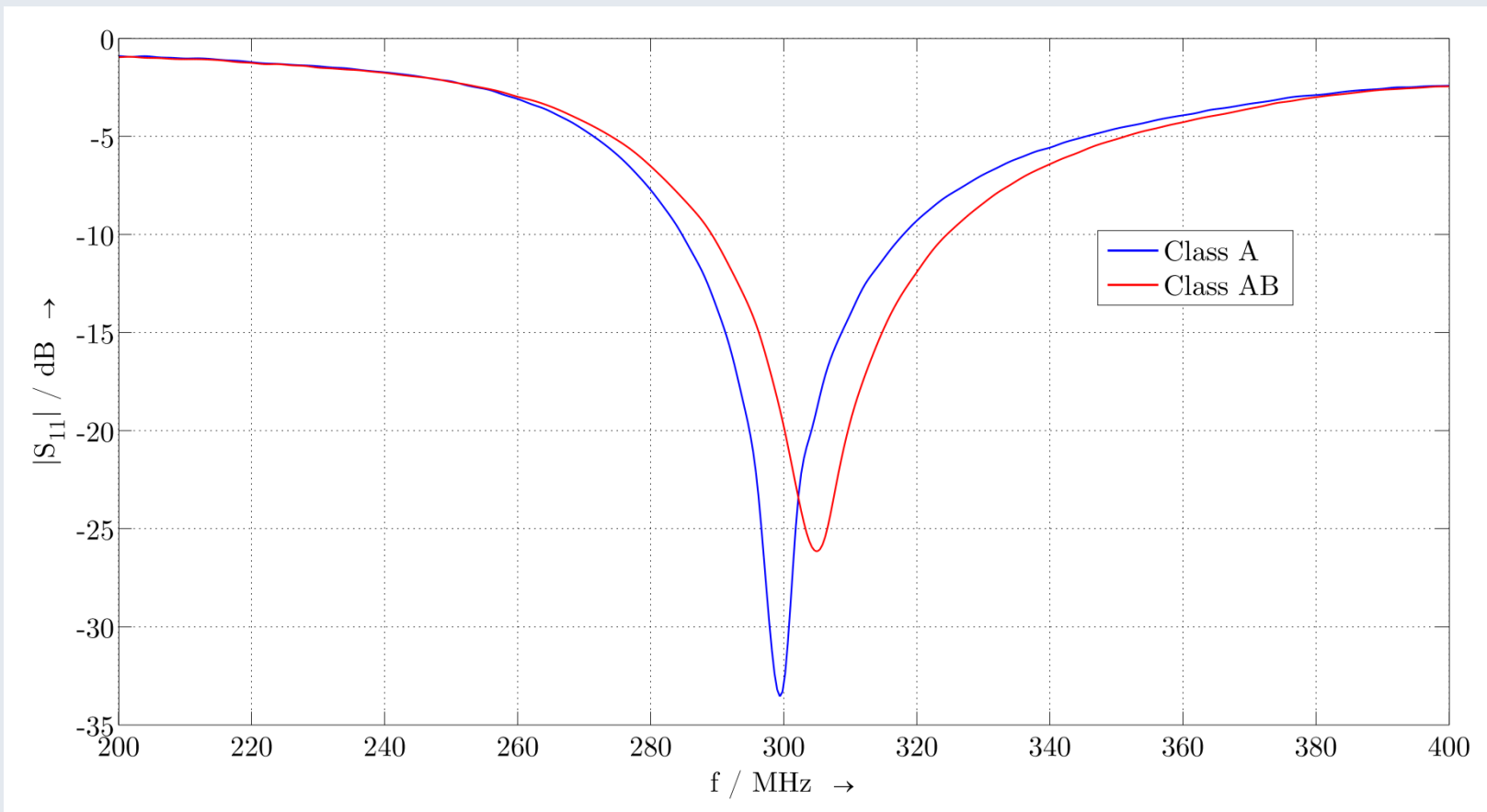
## Input Reflection Coefficient $S_{11}$


- Small signal ( $P_{in} = 0$  dBm) input reflection coefficient  $S_{11}$  as measured with VNA



# Power Amplifier
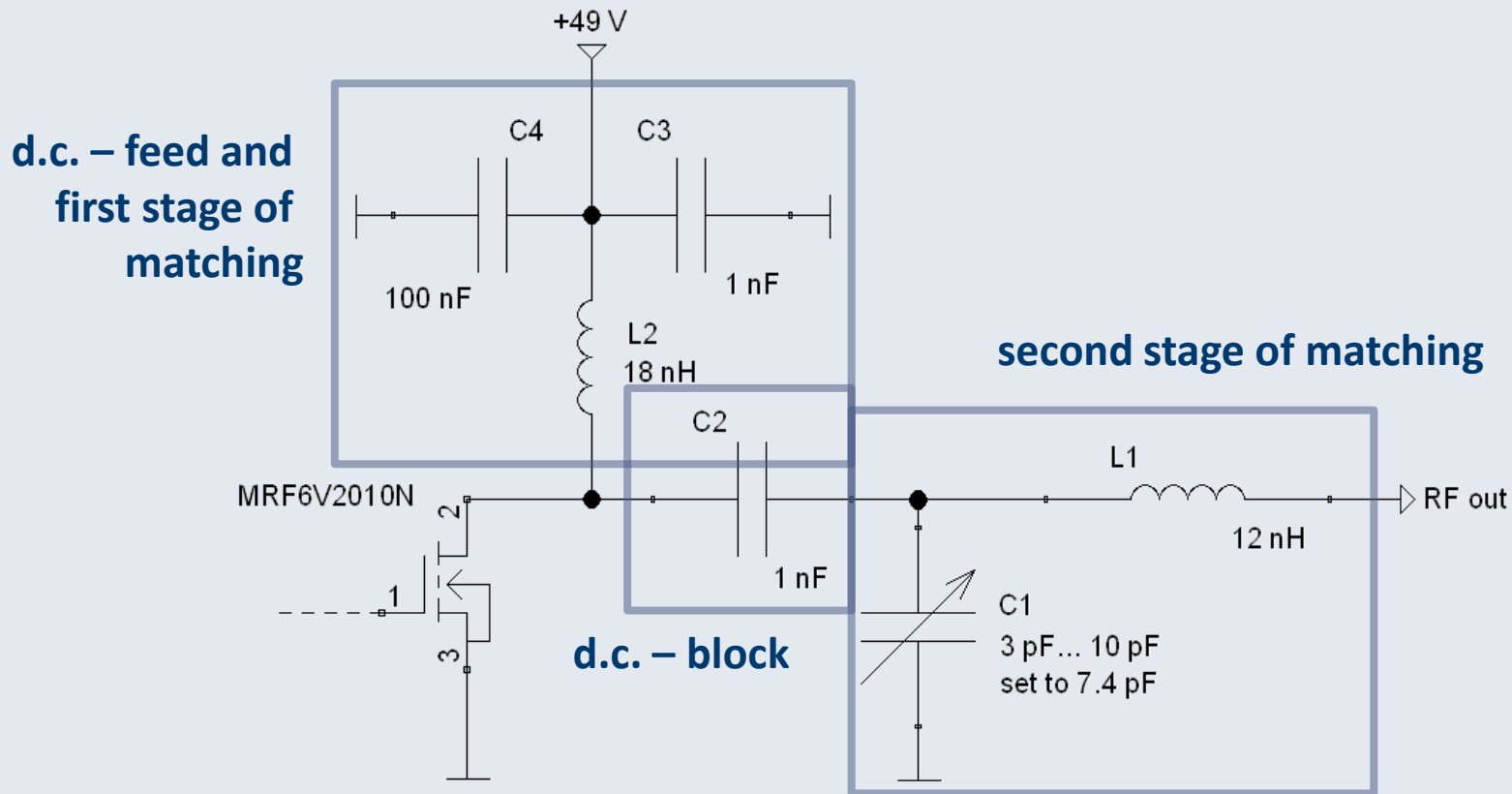
## Output Circuit

- Output circuit provides d.c. – feed and matching of the output of the MOSFET to the 50  $\Omega$  – load



# Power Amplifier


## Power Gain

- Power gain (forward transmission coefficient  $S_{21}$ ) is determined by
  - operating point
  - input power
  - quality of the input and output matching networks
- Power gain has been measured with
  - vector network analyzer (VNA)
  - RF signal generator and power meter
  - (RF signal generator and spectrum analyzer)

# Power Amplifier
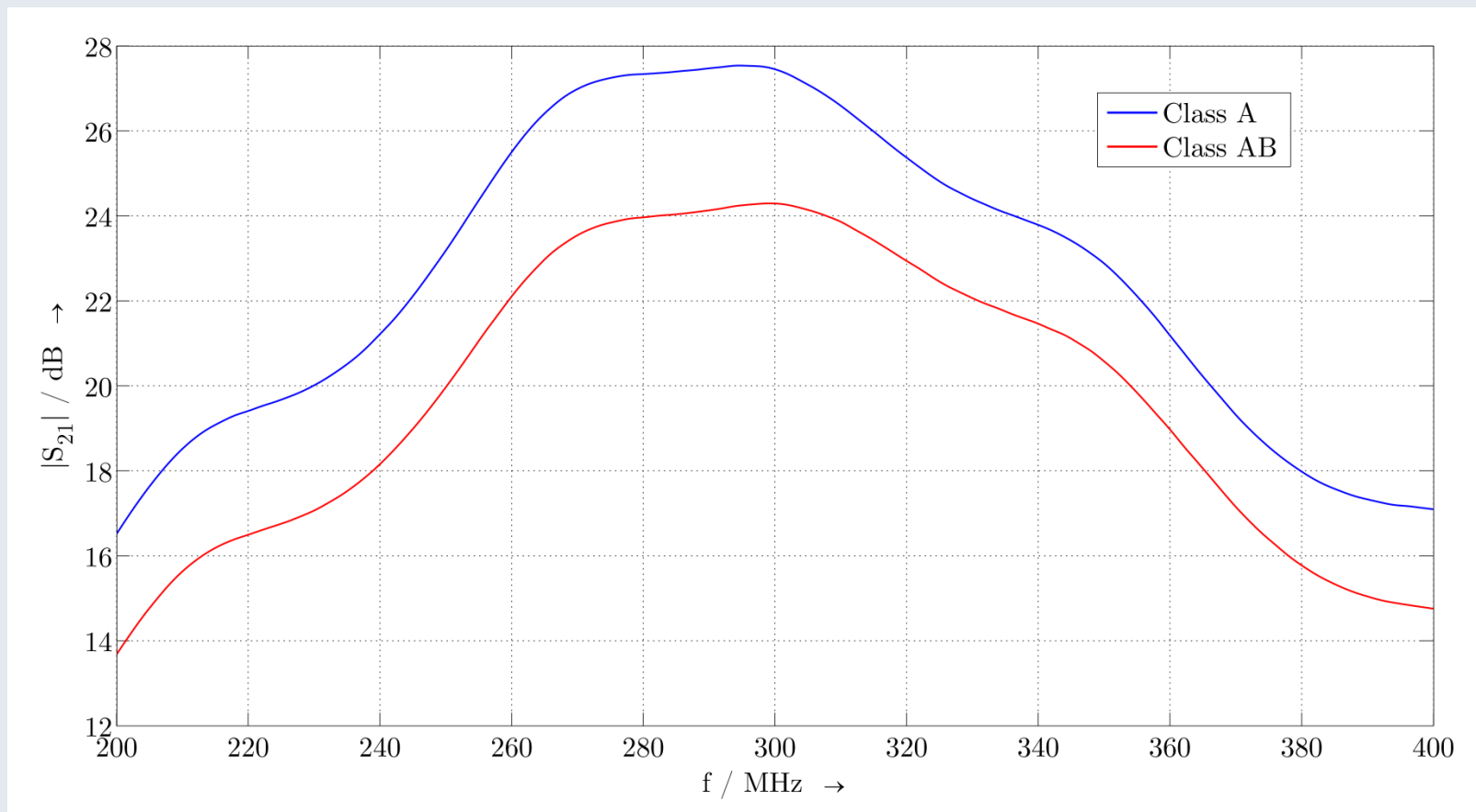
## Power Gain


- Small signal ( $P_{in} = 0$  dBm) power gain  $S_{21}$  as measured with VNA



# Power Amplifier
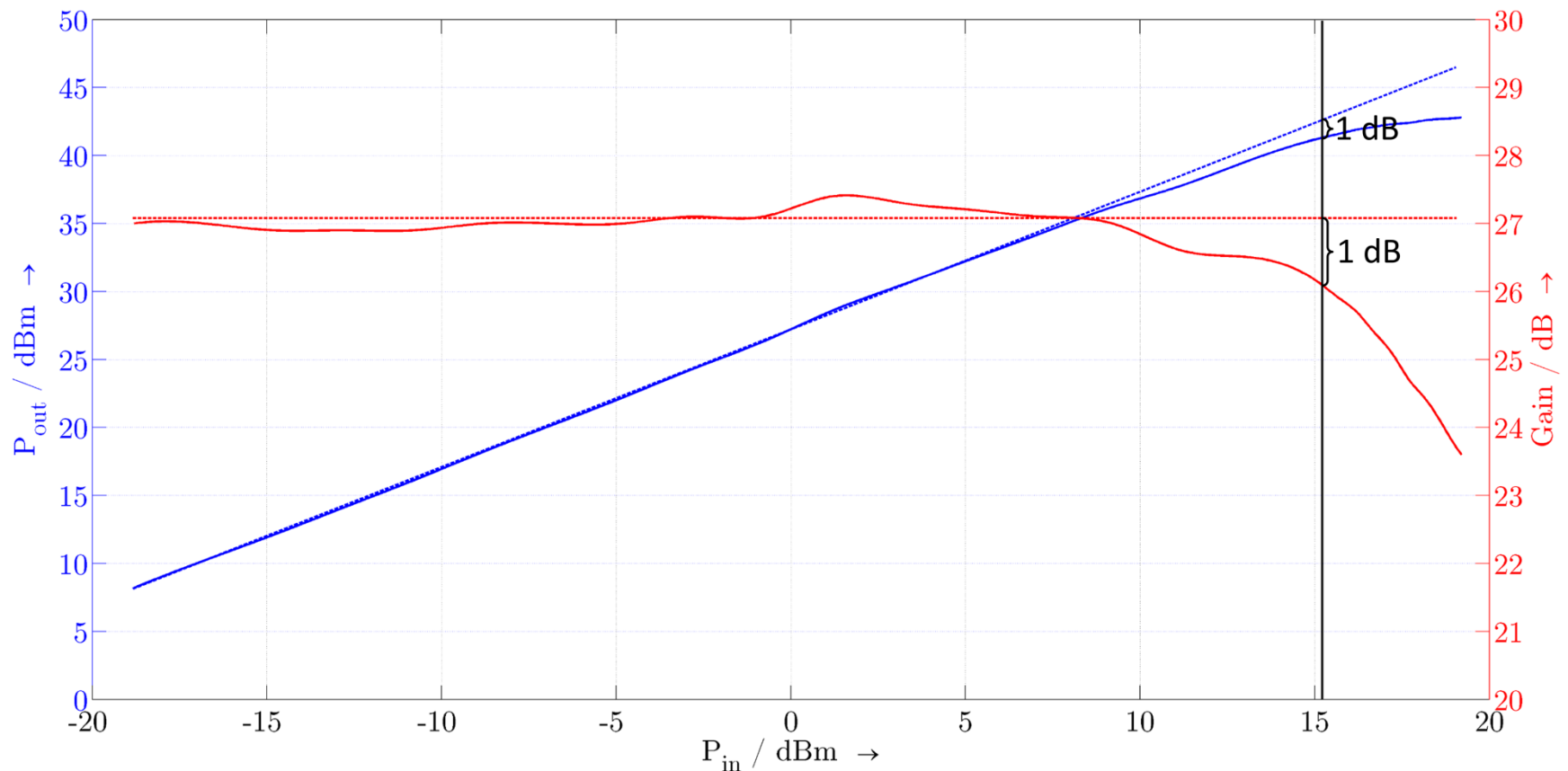
## Power Gain


- Power gain and  $P_{1dB}$  as measured with RF signal generator and power meter



# Power Amplifier

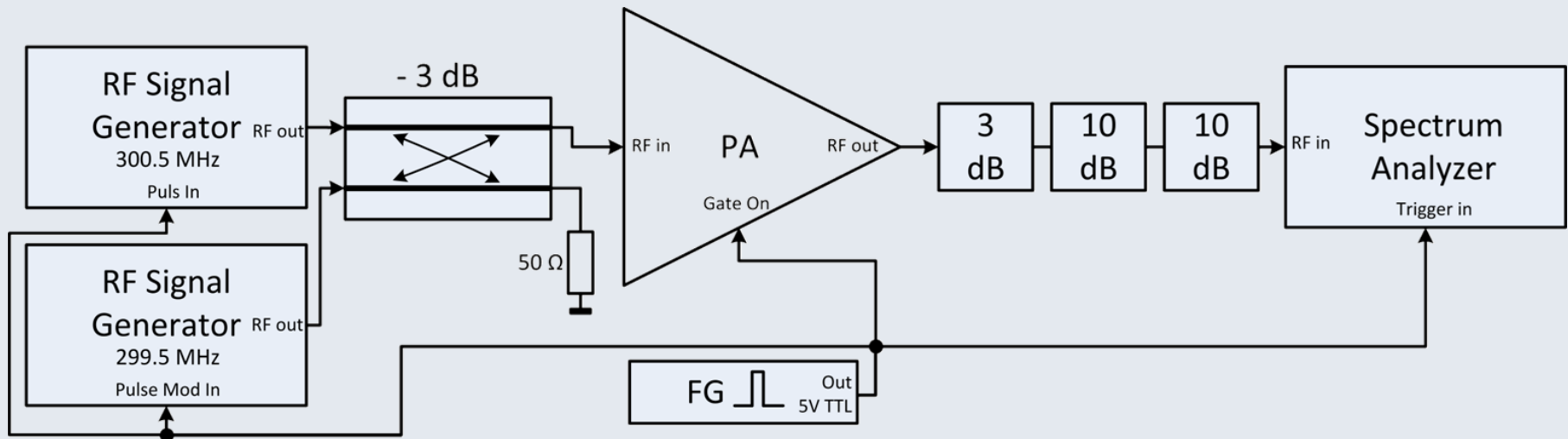
## Intermodulation Distortion

- Third – order intermodulation products are not affected by output filter, so they can be used to quantify the harmonic distortion caused by the MOSFET.
- Third – order intercept point has been measured with a two – tone measurement:



# Power Amplifier

## Intermodulation Distortion

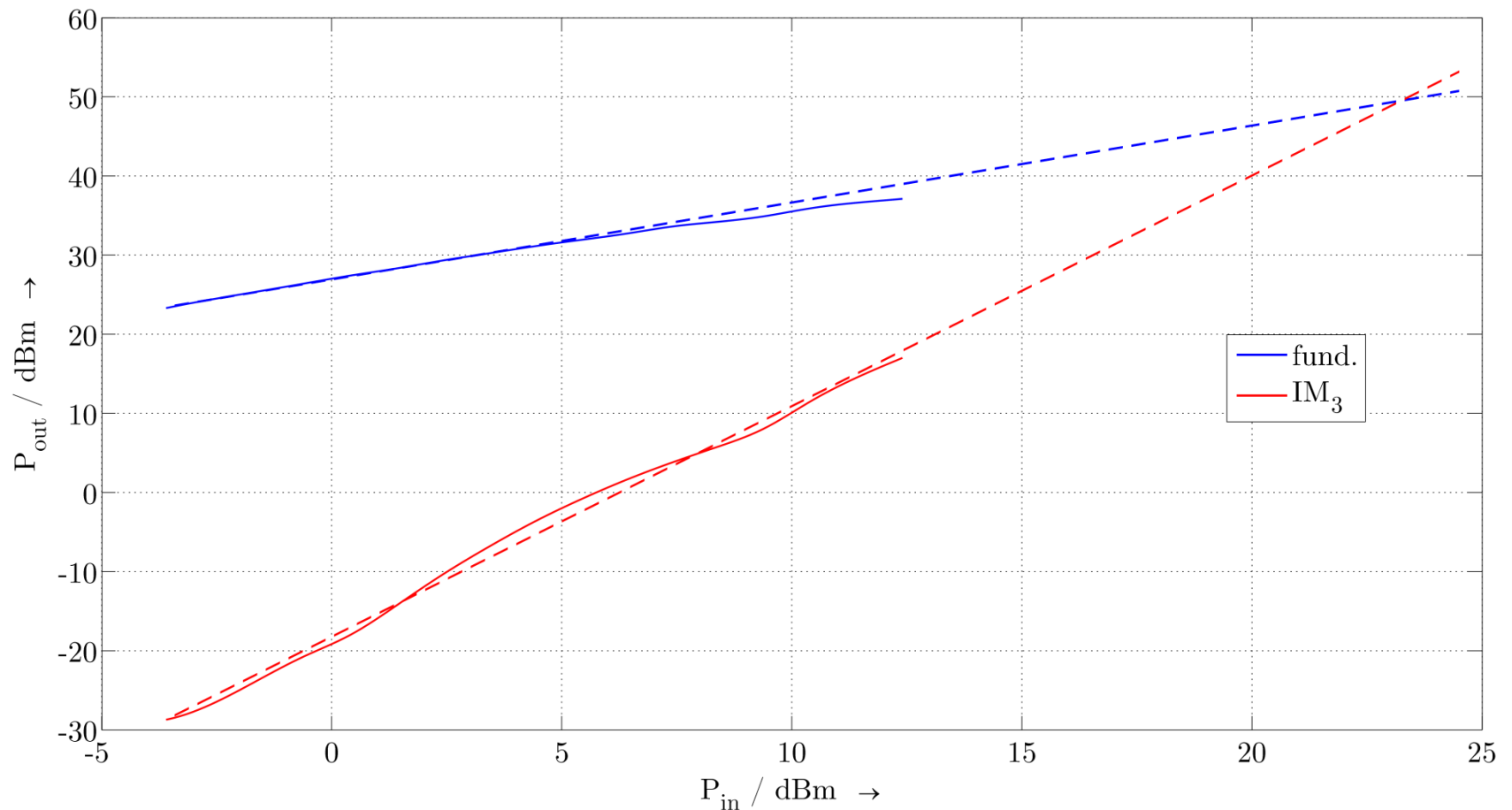

# Power Amplifier

## Summarized Data


	VNA	Power Meter	Spectrum Analyzer	Datasheet
<b>Input Reflection Coefficient <math>S_{11}</math></b> ( $P_{in} = 1 \text{ mW} / 0 \text{ dBm}$ )	- 33 dB		<b>These values need some discussion!</b>	
<b>Small signal power gain</b> ( $P_{in} = 1 \text{ mW} / 0 \text{ dBm}$ )	27.5 dB	27.1 dB		ca. 24 dB
<b><math>P_{1dB}</math></b>		15.2 dBm		ca. 17.3 dBm
<b>Maximum Output Power</b> ( $P_{in} = 100 \text{ mW} / 20 \text{ dBm}$ )		19.1 W / 42.8 dBm		12.6 W / 41 dBm
<b>IIP<sub>3</sub></b>			23.2 dBm	
<b>OIP<sub>3</sub></b>			49.5 dBm	



- Small signal power gain and maximum output power strongly exceed the values to be expected from the datasheet.
- Explanations:
  - Measurements have been performed with three different principles, leading to similar results → plausible
  - Measurements at  $V_{GS} = 3.4$  V (Class A); datasheet values at  $I_{DQ} = 30$  mA (corresponding to  $V_{GS} \approx 2.6$  V; close to Class B)
  - Measured input return loss  $S_{11}$  is approx.  $-33$  dB; datasheet values are between  $-14$  and  $-9$  dB
  - Input and output matching networks are quite different from the networks in the datasheet, both in architecture and component values
- realized matching networks are supposedly better than the manufacturer's

# Gate Bias Circuit

## Concept

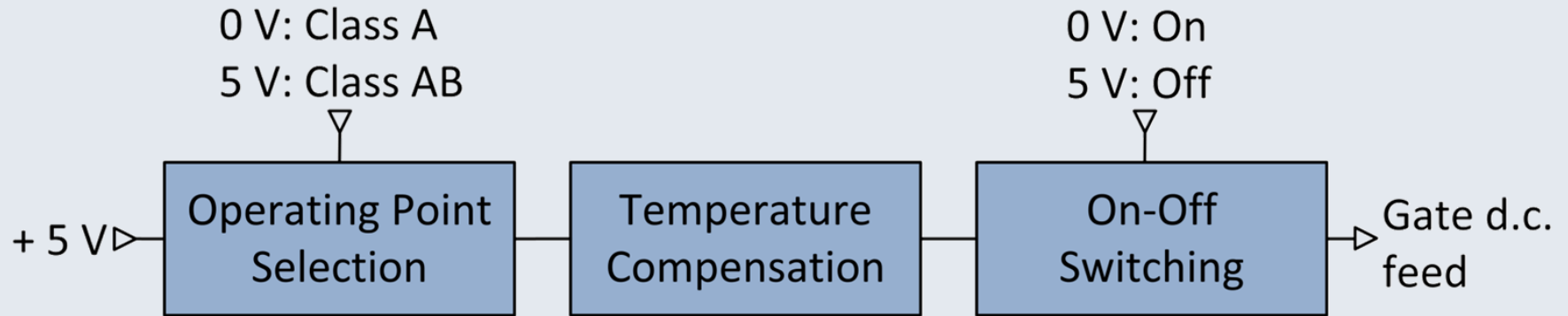


- Operating Point Stabilization
- Choosing a Class A and a Class AB operating point
- Switching between these two points

Temperature stabilization of the quiescent current

Fast switching between the designated gate bias voltage and  $V_{GS} = 0\text{ V}$

# Gate Bias Circuit

## Operating Point Selection

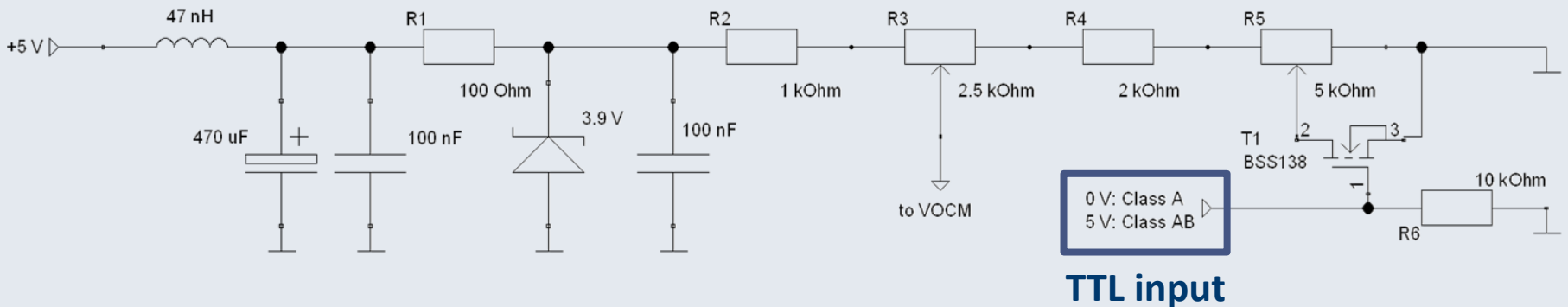


- Input voltage is stabilized against ripple and noise on the power supply rail with low-pass filter and Zener diode.
- One potentiometer ( $R_3$ ) allows the selection of the Class A operating point.
- A portion of a second potentiometer ( $R_5$ ) is bypassed by a logic-level MOSFET T1 when a voltage of 5 V is applied at its gate.
- This potentiometer determines the distance between the Class A and the Class AB operating point.

# Gate Bias Circuit
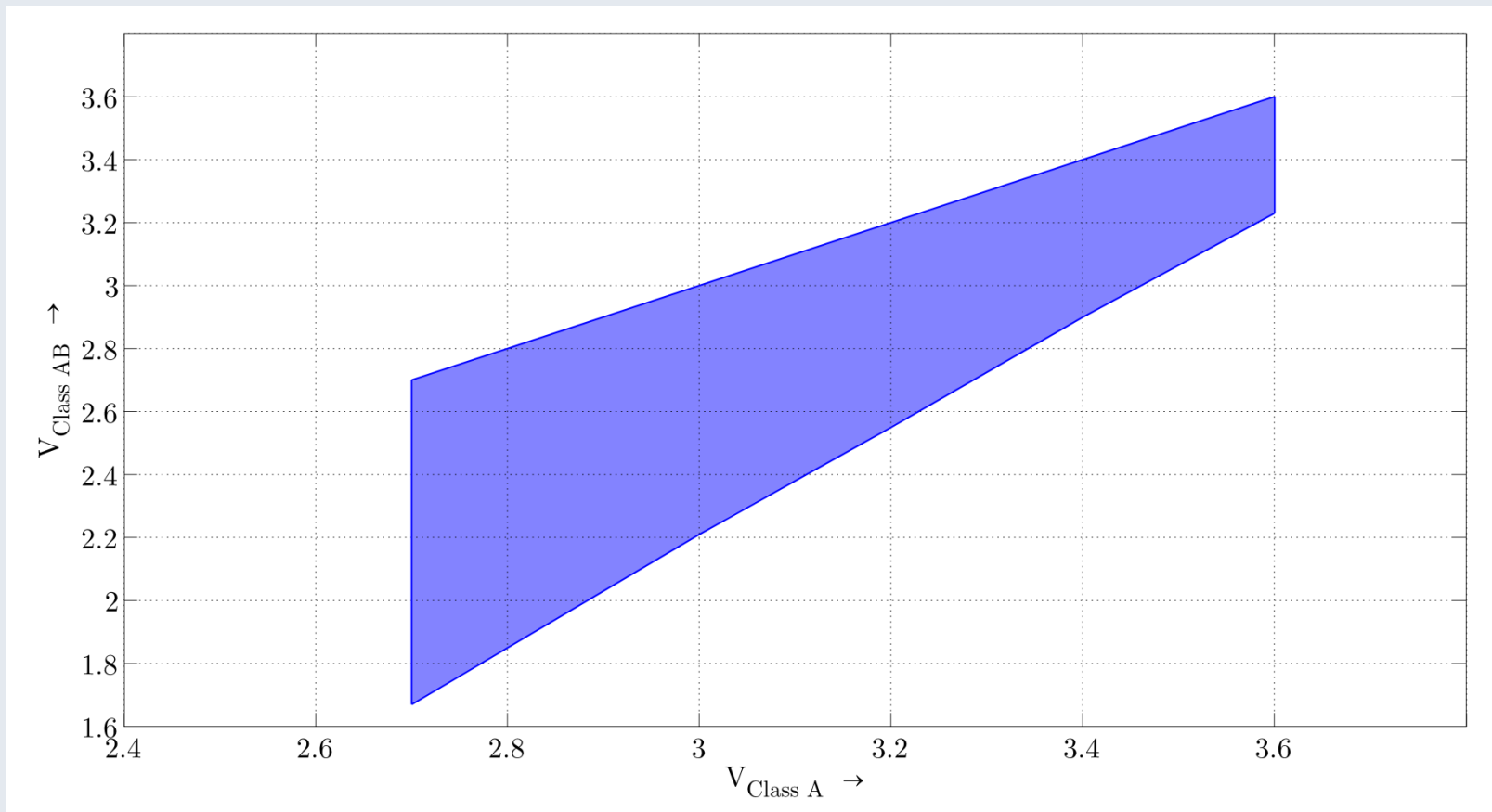
## Operating Point Selection


- Only certain pairs of operating points can be reached with this circuit



# Gate Bias Circuit
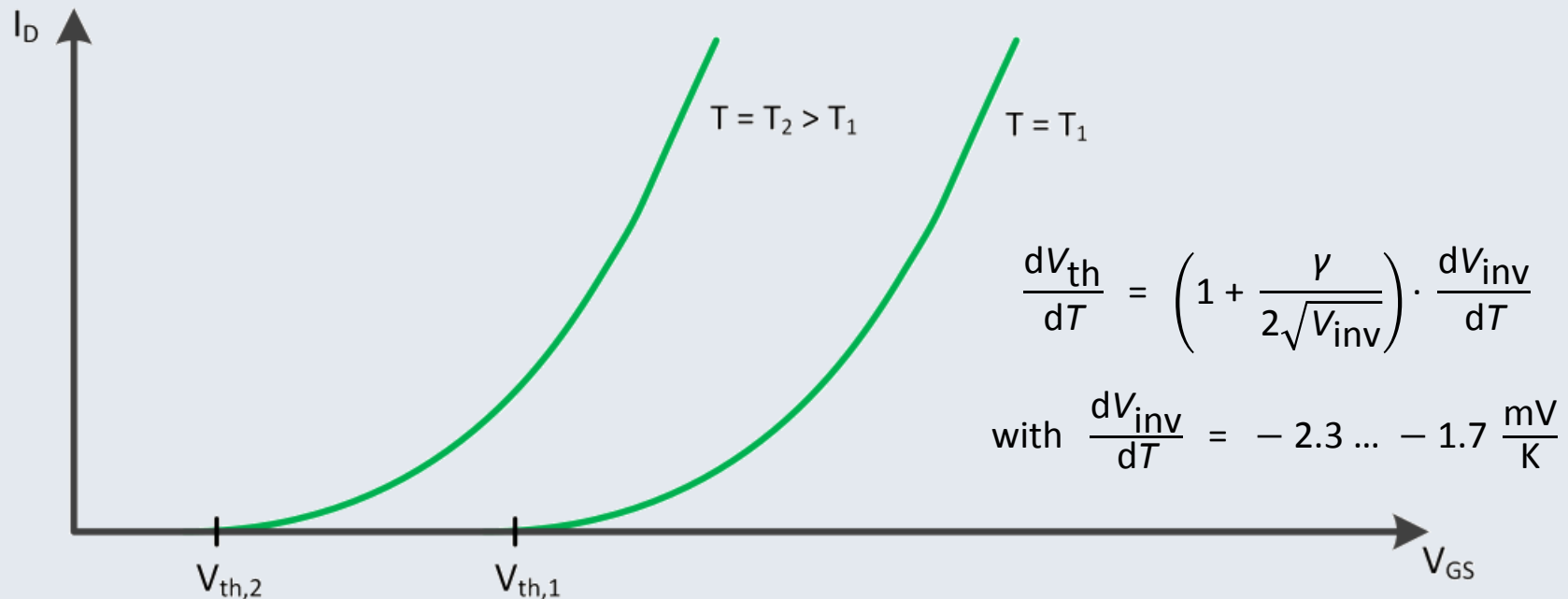
## Temperature Compensation

- The threshold voltage of a MOSFET decreases with increasing temperature → the quiescent drain current increases.



- The operating point shifts as the device heats up.

# Gate Bias Circuit


## Temperature Compensation

- The forward voltage  $V_D$  of a silicon pn–diode follows a similar law as the threshold voltage of a MOSFET:  $\frac{dV_D}{dT} \approx -1.7 \frac{\text{mV}}{\text{K}}$
- Compensation principle:
  - one pn–diode is placed far away from the MOSFET (approximately ambient temperature)
  - one pn–diode is placed close to the MOSFET (approximately junction temperature)
  - The difference between the forward voltages is amplified and added to the selected gate bias voltage by a differential amplifier with common mode offset input of type AD8137

# Gate Bias Circuit

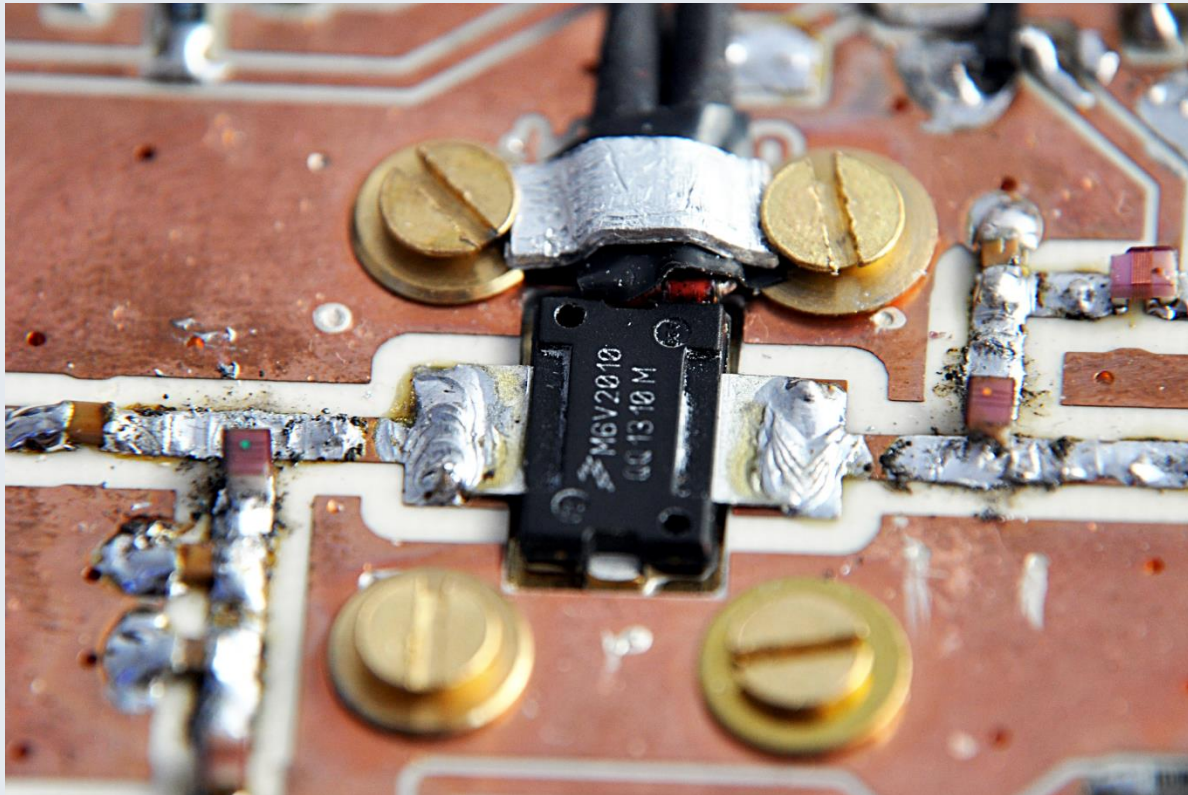
## Temperature Compensation

- Sensor diode is placed next to the MOSFET, not on top because diode picks up electromagnetic field radiated by the MOSFET



# Gate Bias Circuit

## Temperature Compensation

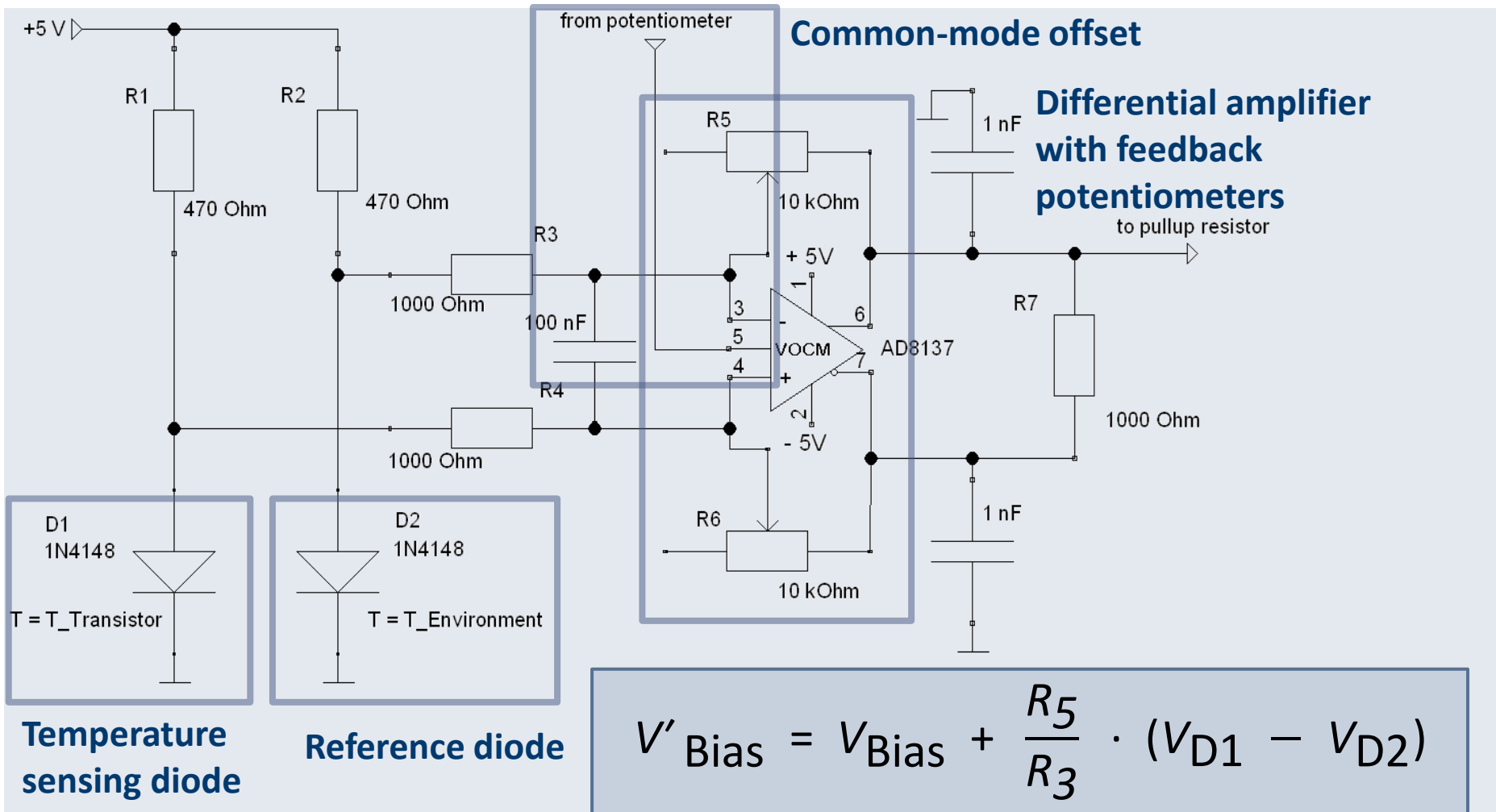



# Gate Bias Circuit


## Temperature Compensation

- The feedback potentiometers around the differential amplifier must be set to the same value for the common mode offset to work properly
- A procedure for adjusting the feedback resistors for optimum temperature compensation has been developed.
- The quiescent drain current is held constant to within about 10 mA.
- Problem: In an enclosure the reference diode will eventually heat up, too.

# Gate Bias Circuit
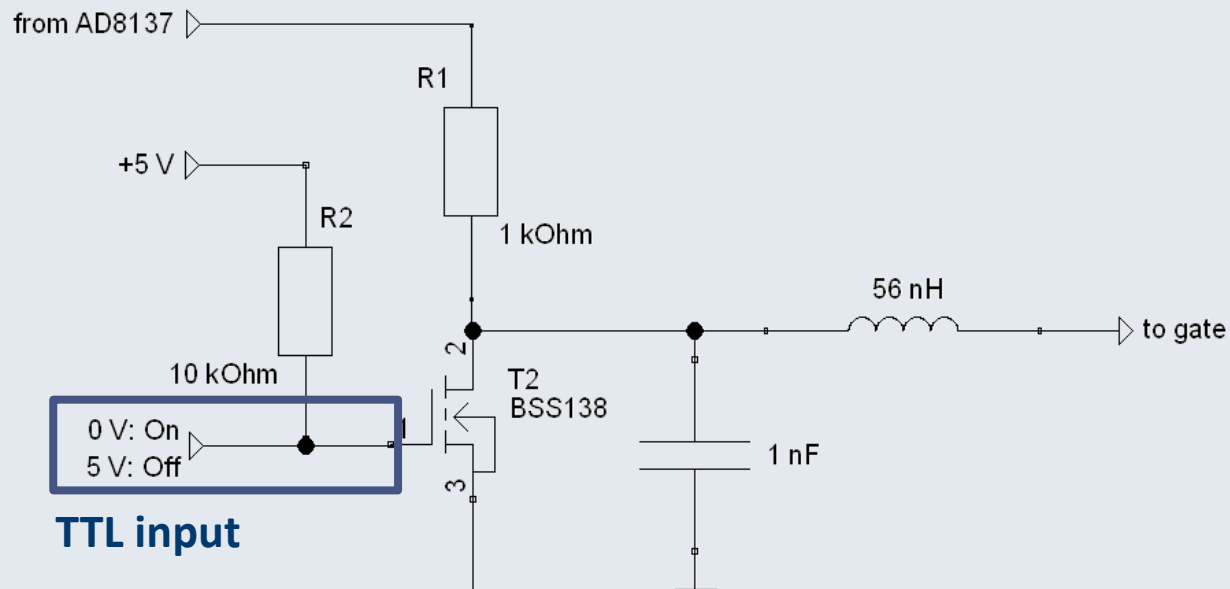
## On-Off Switching

- Pulsed operation: amplifier does not need to be in its operating point when no pulse is present at the RF input
- Power dissipated in the MOSFET can be reduced by switching  $V_{GS}$  to 0 V between the pulses.




# Voltage Regulator

## Concept

- Power amplifier needs stable drain–source voltage, especially during the RF pulses
  - Little current flowing into the drain between the pulses
  - Significant current flowing into the drain during the pulses
    - Large transients
    - Power supply regulator is under stress
    - Power line inductance hinders transients
    - Power supply might not be able to provide the required drain current
- **Solution:** charging capacitors and discrete voltage regulator close to the amplifier


# Voltage Regulator Circuit

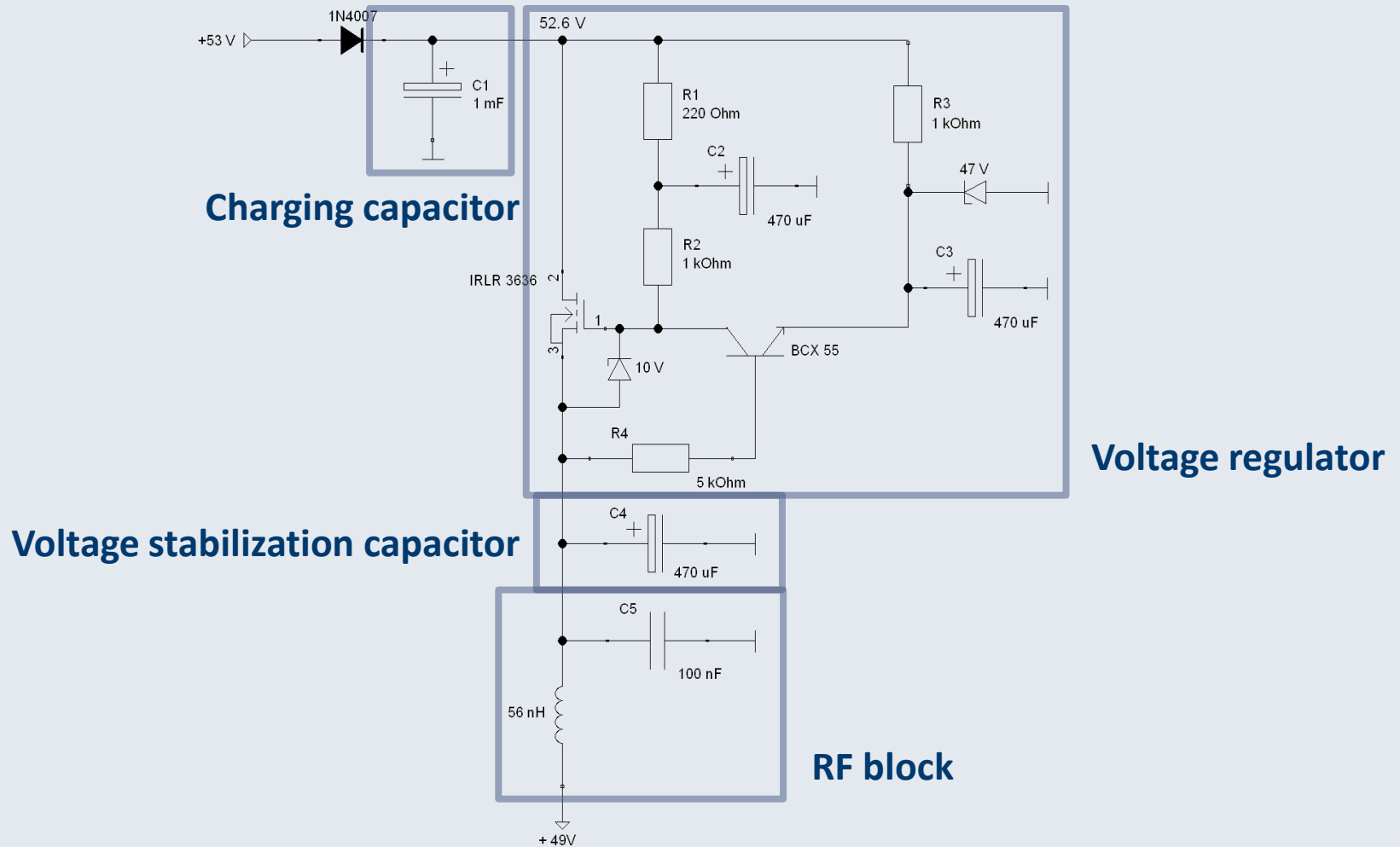

# Voltage Regulator
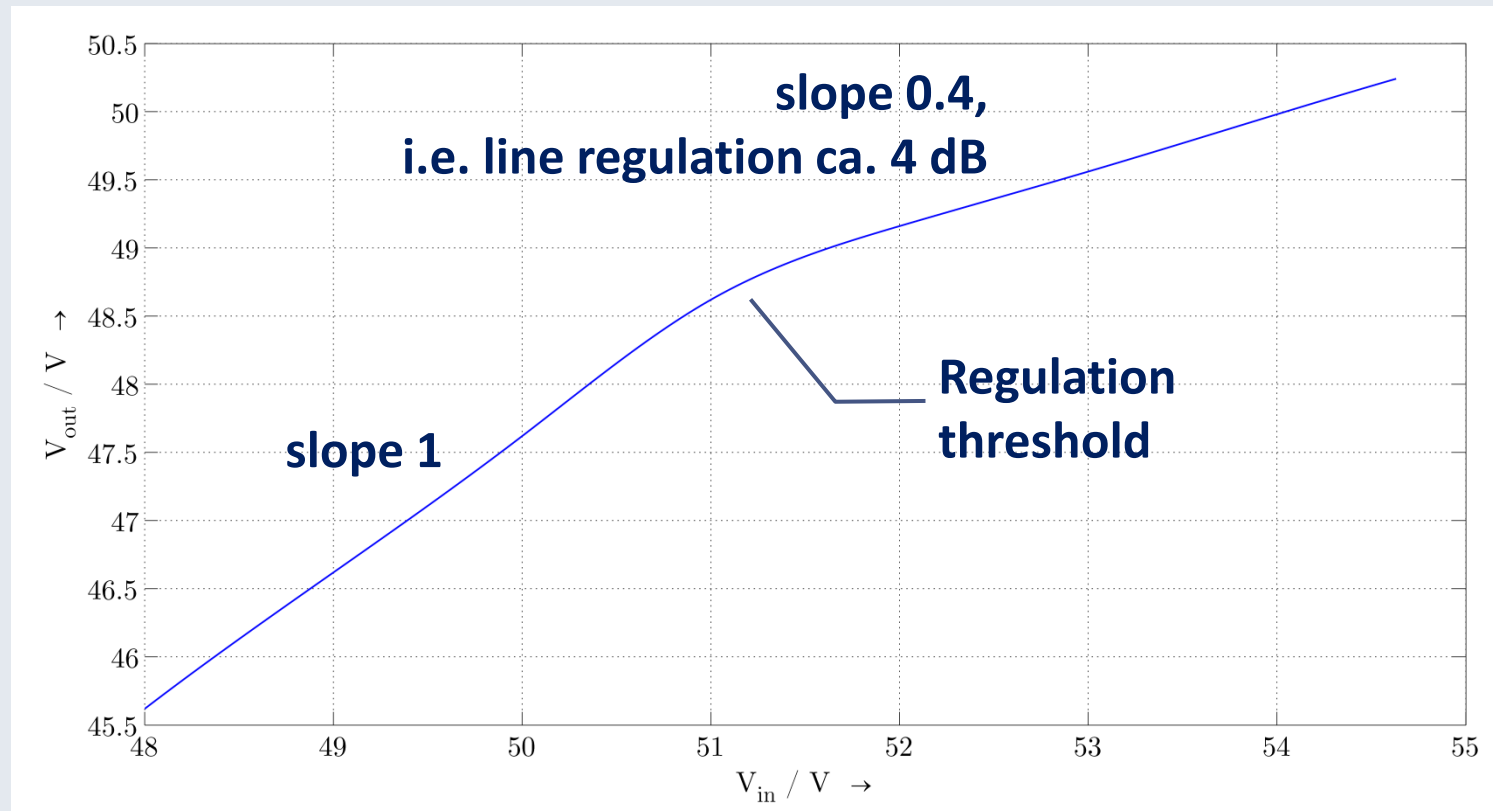
## Static Line Regulation


- Static line regulation: dependence of the output of a regulator on the input in the static case



# Voltage Regulator
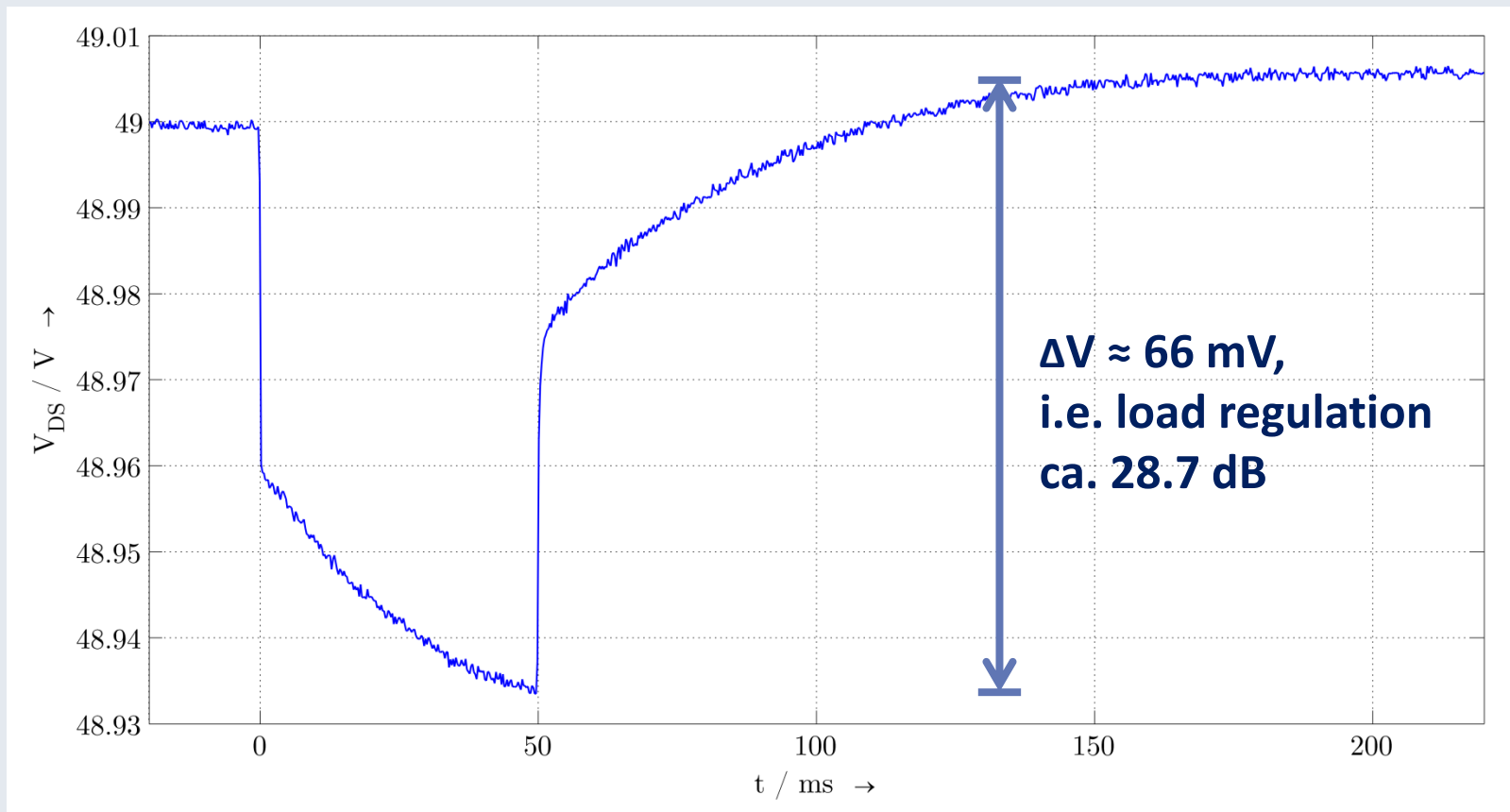
## Load Regulation

- Load regulation: dependence of the output of a regulator on the load



- Necessity to measure the output power of the amplifier during operation
- Difficult because of high frequency and large dynamic range
- Solution: AD8307 logarithmic amplifier
  - converts RF voltage to d.c. voltage (envelope)
  - outputs a voltage that is proportional to the logarithm of the input voltage
- Theoretically output power can be measured with a multimeter this way

# Power Monitor

## Concept


- Output voltage of the driver amplifier needs to be reduced to within the input range of the AD8307 with a probe circuit

Probe resistor with frequency compensation

a.c. coupling

50  $\Omega$  termination


Input equivalent circuit of the AD8307

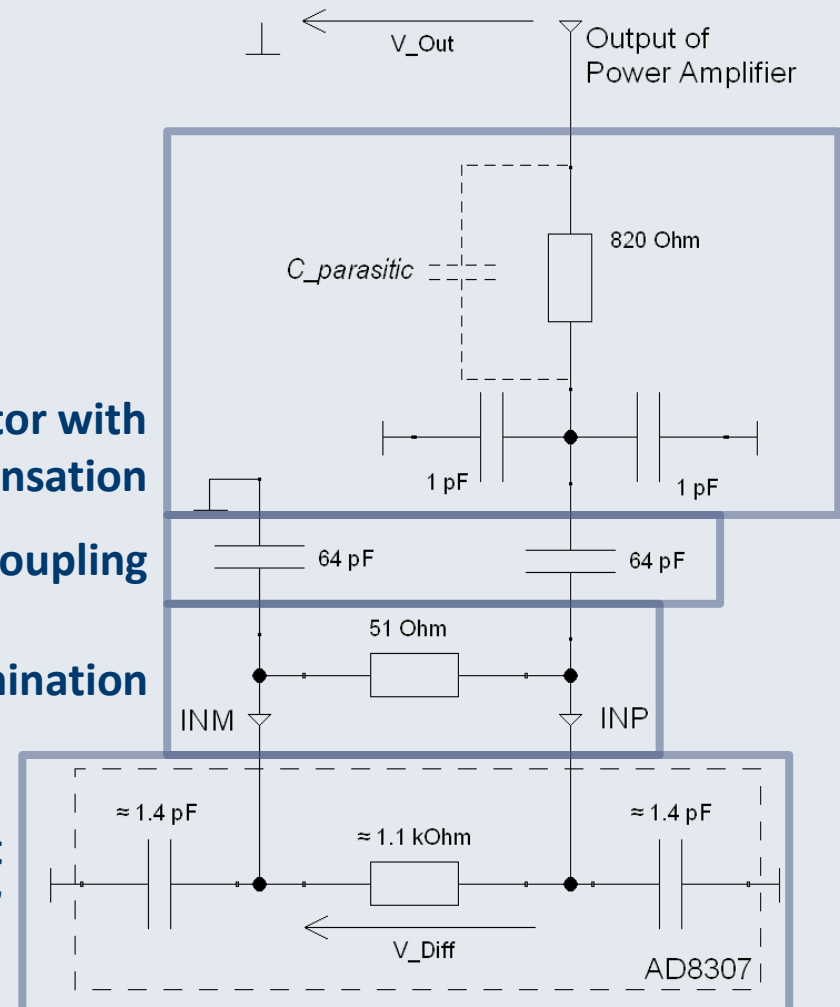




# Power Monitor

## Frequency Response

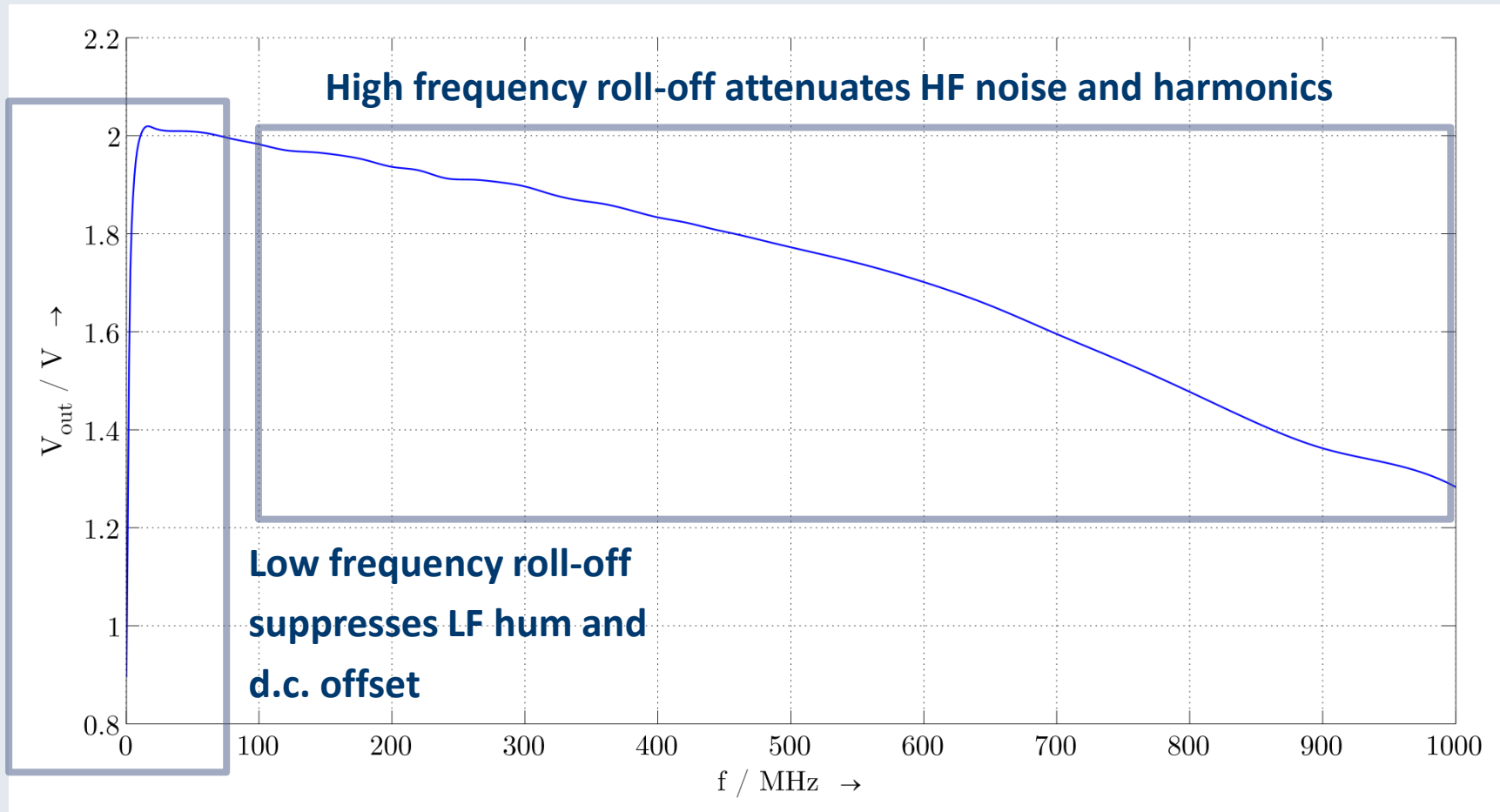


# Power Monitor

## Pulsed Operation

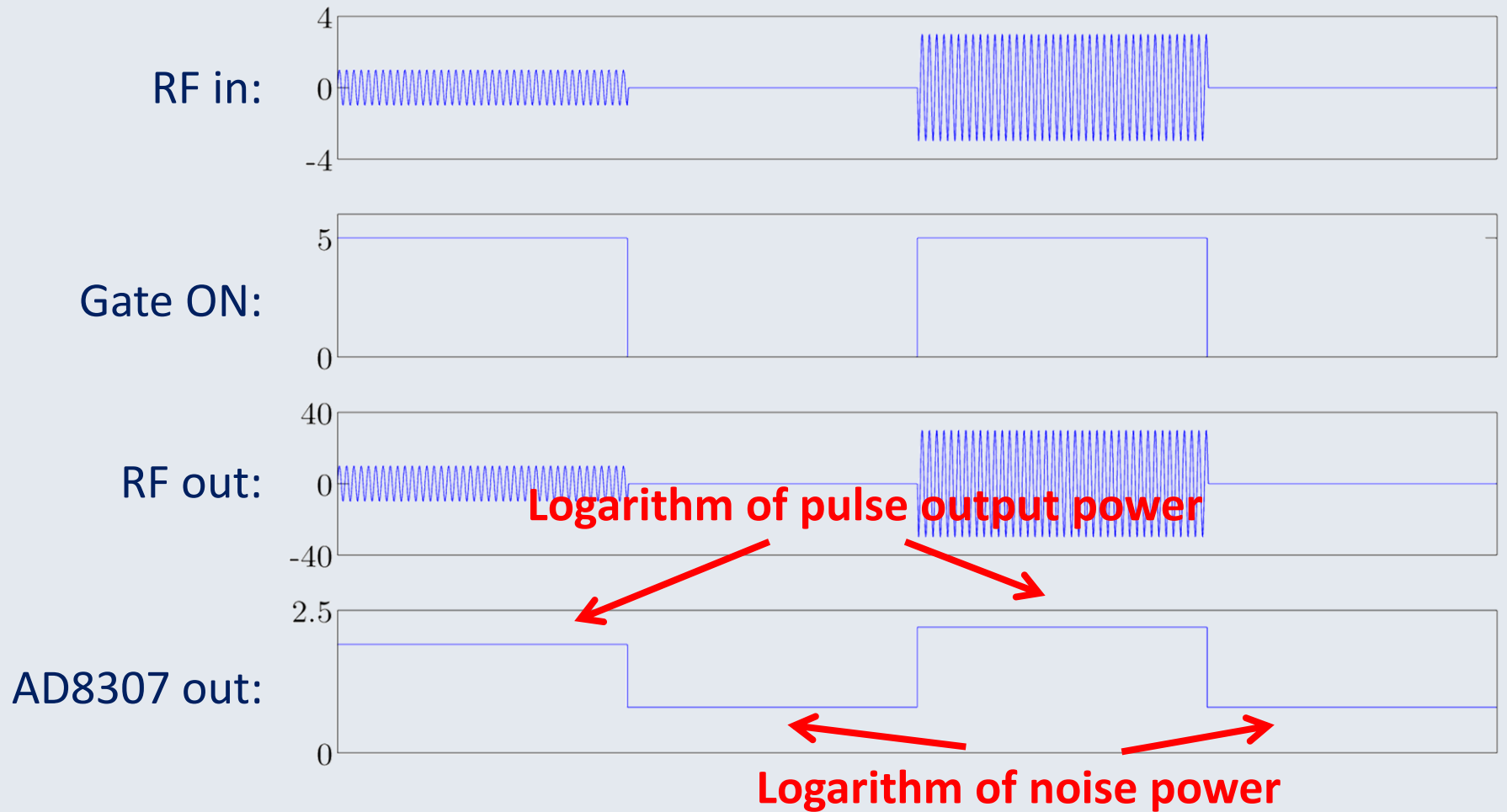

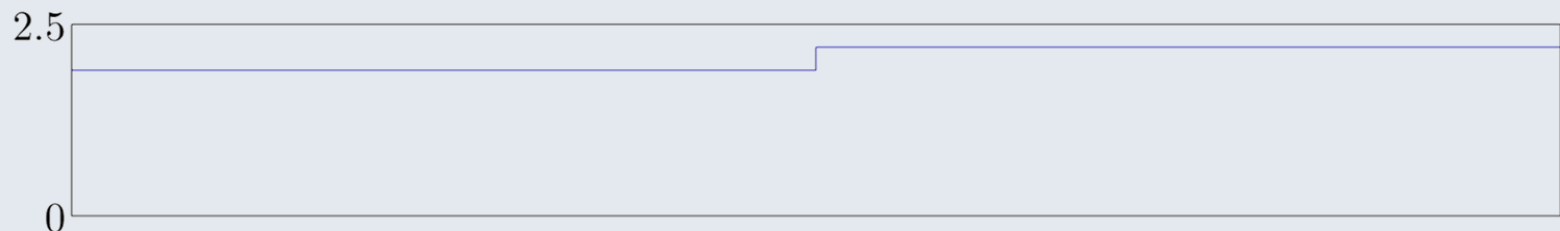- Consequence for measurement of output power:
  - Analog multimeter: approx. measures average power
  - Oscilloscope: measures pulse and noise power
  - Digital multimeter: does not allow any sensible measurement
- Solution: Sample-and-hold circuit based on an LF398 that holds the output voltage of the AD8307 between the pulses




- S/H circuit can be controlled by “Gate ON” voltage because it is supposed to be high only during the RF pulses



# Power Monitor
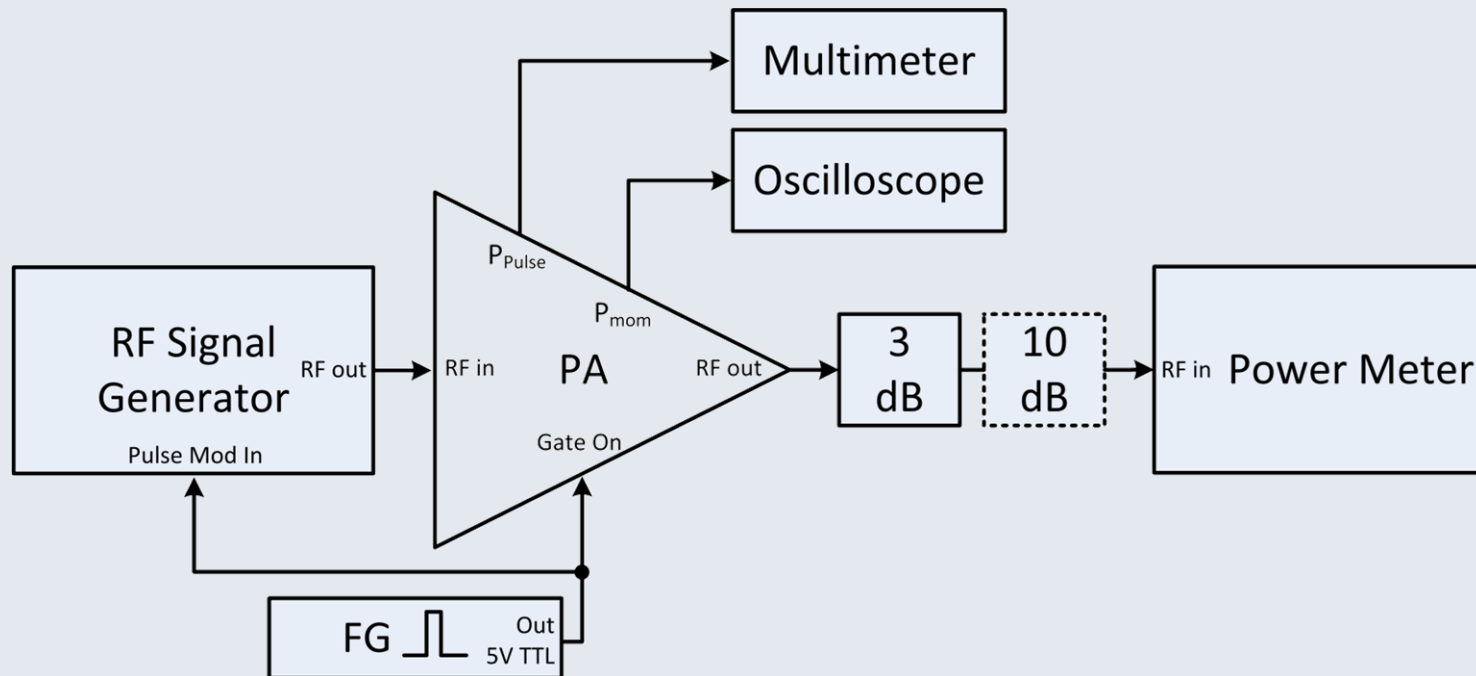
## Calibration


- Relationship between d.c. output voltage and output power must be established
- Calibration against a reference power meter



# Power Monitor
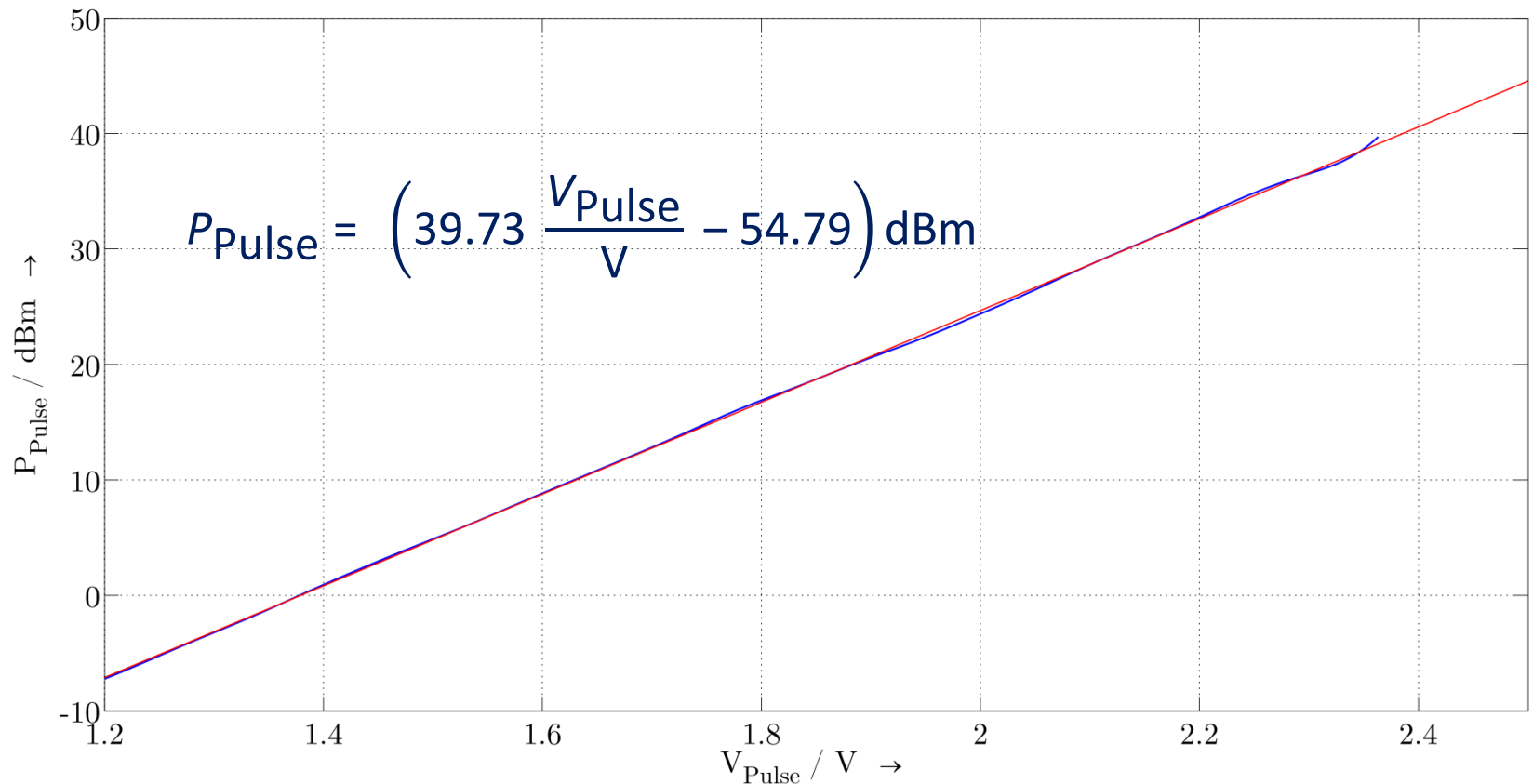
## Calibration

- Linear law between d.c. output voltage and power in dBm:




# Assembly

## Circuit Board Layout

Voltage Regulator



Power  
Amplifier

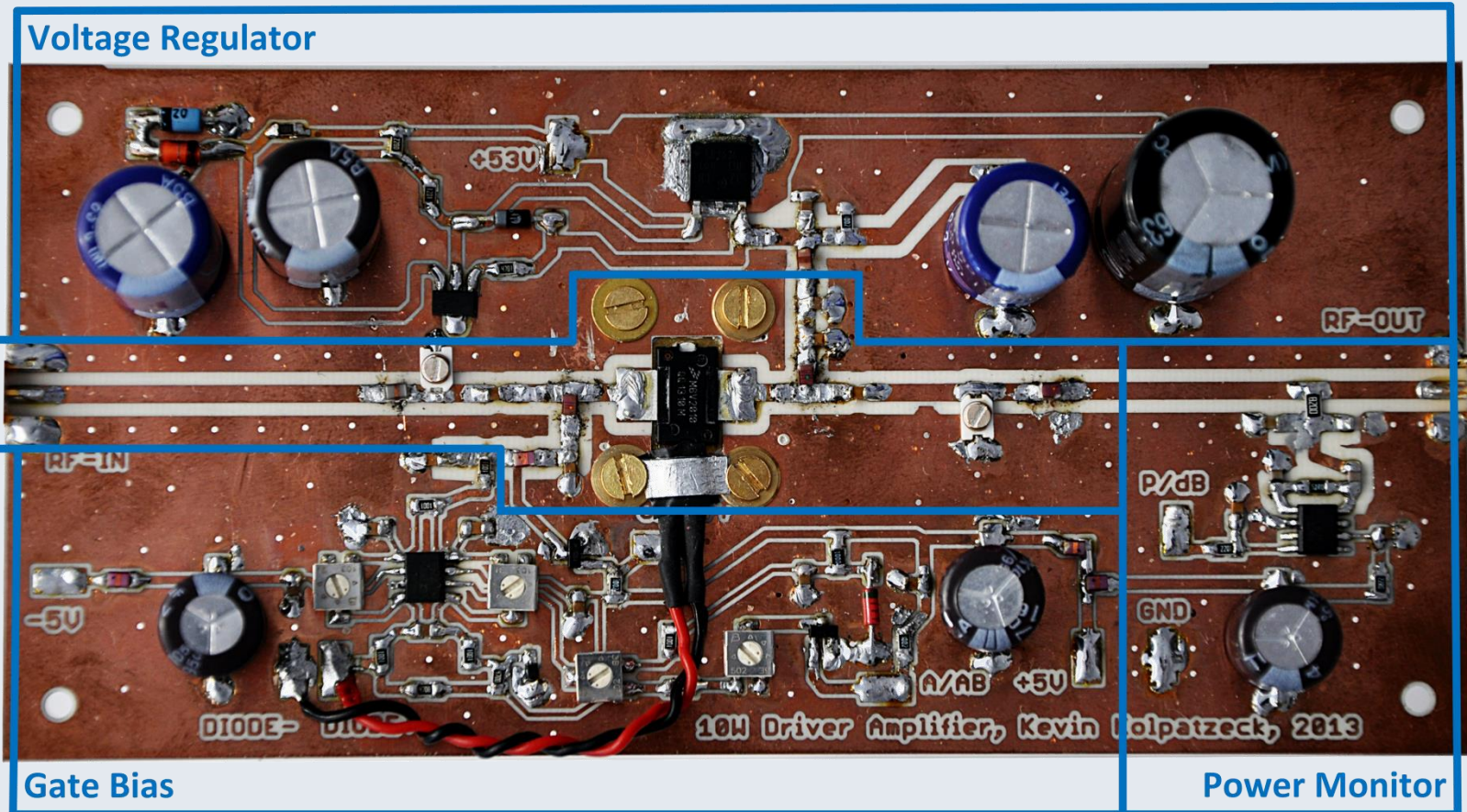

# Assembly
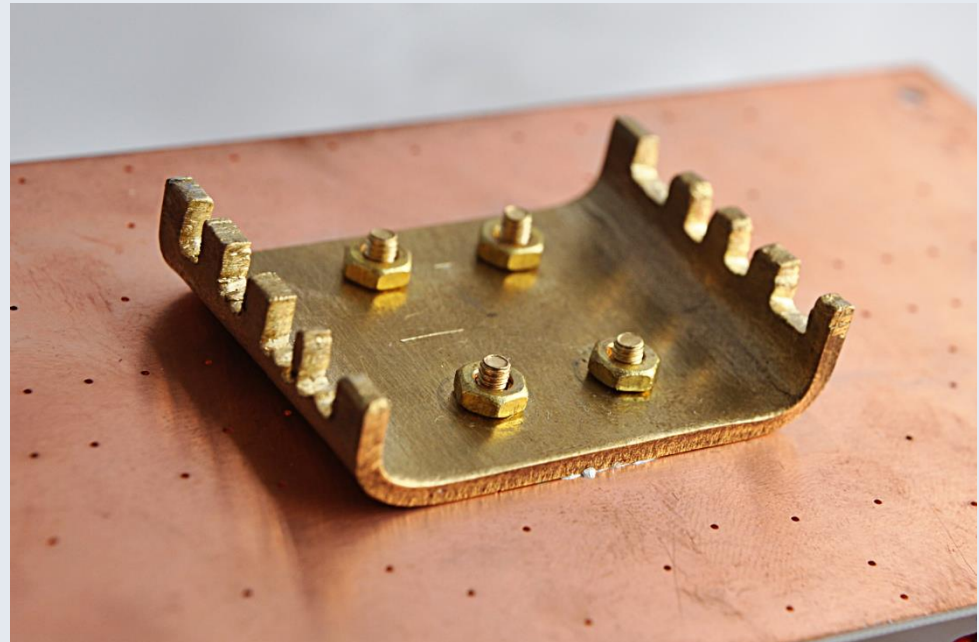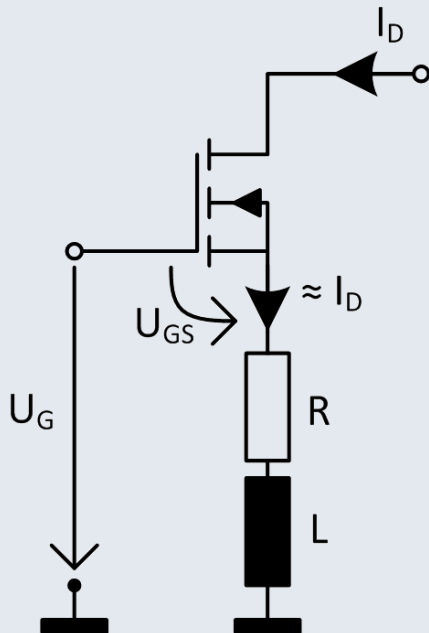
## Power MOSFET Mounting


- Good source–ground connection (low resistance, low inductance) and low thermal resistance is important
- Glue–on mounting on a self–built brass heatsink






# Assembly

## Power MOSFET Mounting

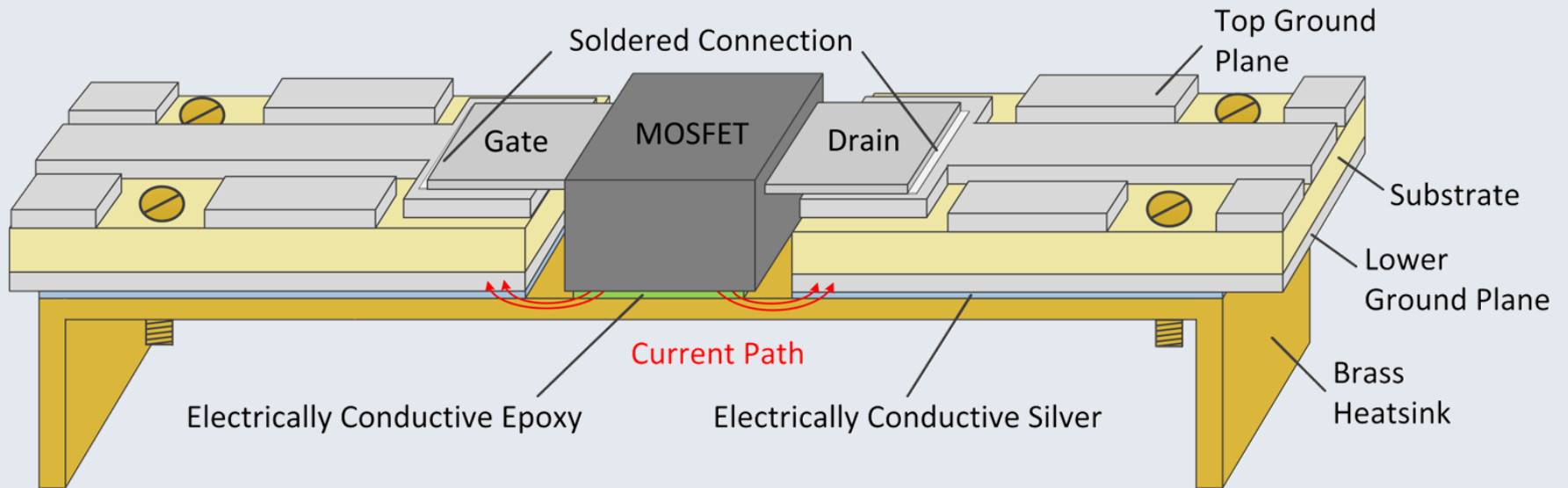

# Assembly


## Housing

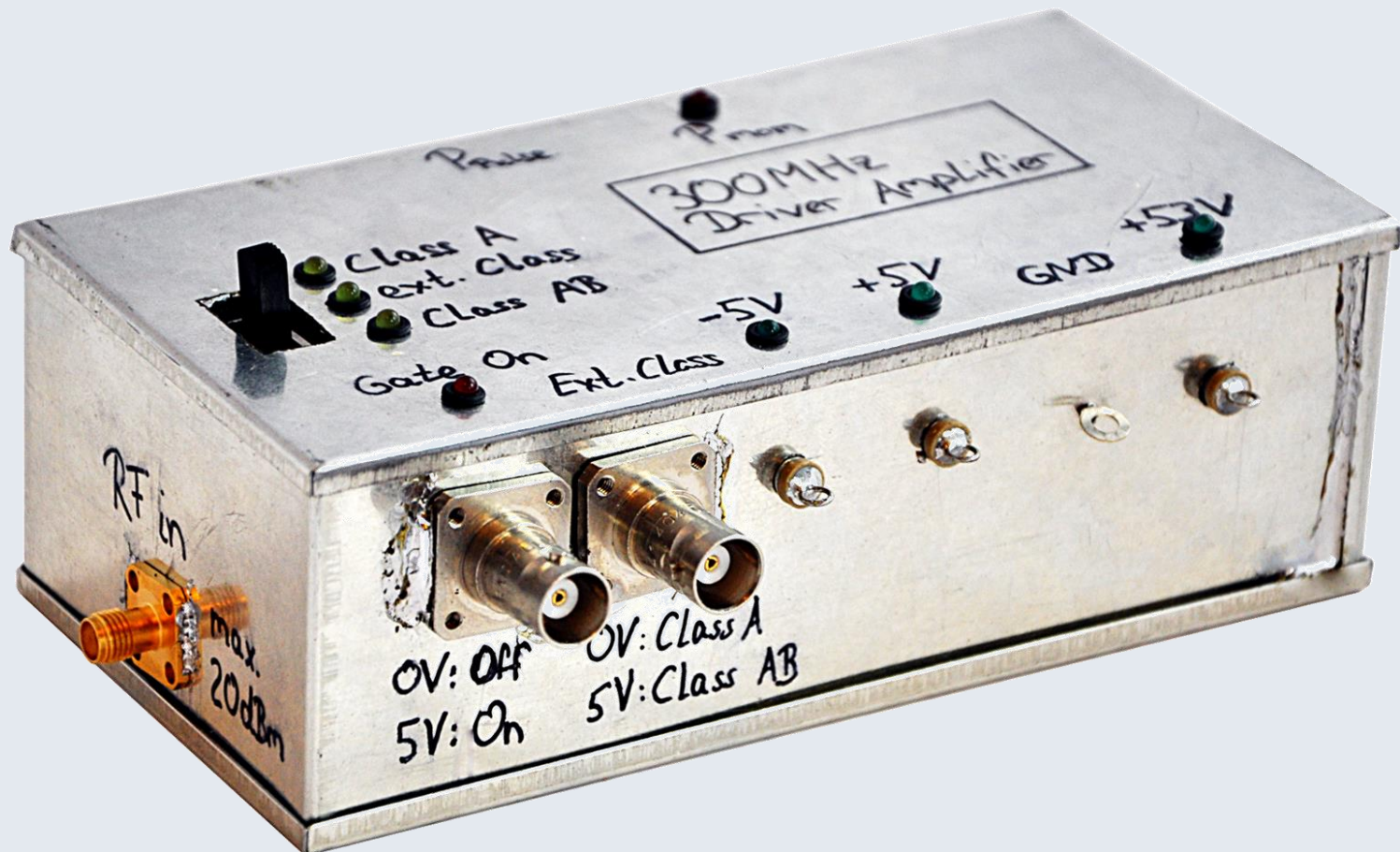

# Assembly

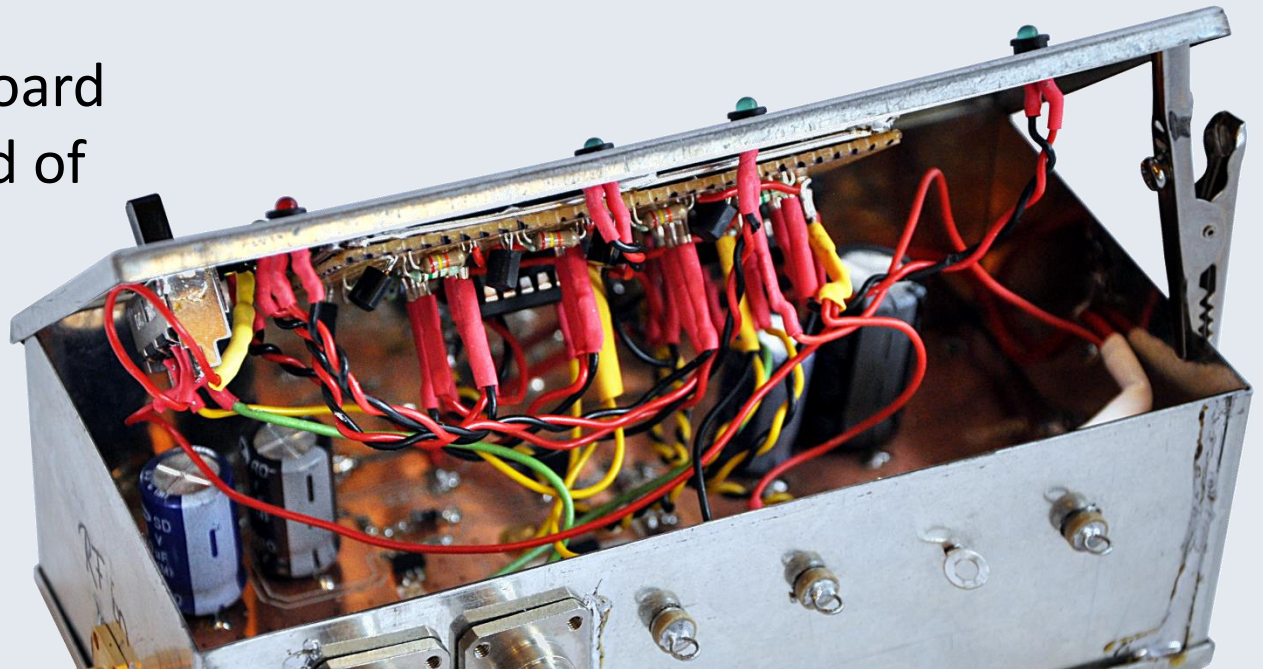
## Additional Circuitry

- Signaling LEDs
- Inverter for the Gate ON voltage
- Polarity protection
- Placed on a perfboard underneath the lid of the box


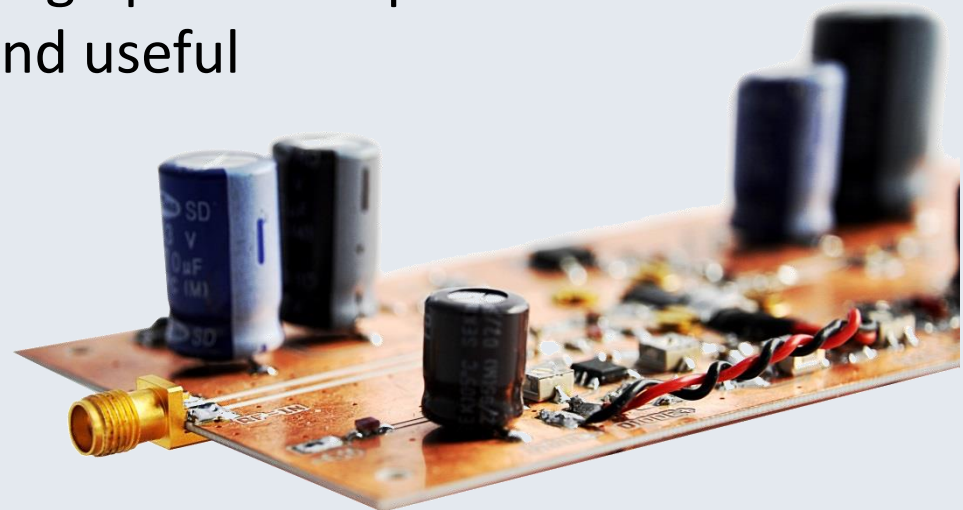
# Conclusion

- Complete, conveniently usable amplifier for amplification from 100 mW to 10 W
- Amplification and maximum output power higher than expected
- Relatively poor distortion figures
- Concepts for use in driver and high power amplifier have been tested and proven functional and useful
  - Operating point flexibility
  - Temperature compensation
  - Gate shutdown
  - Power Monitor



Thank you for your interest!