

Development of a 24GHz fully integrated VCO

Saeid Ghassemi

Supervisors:

Dipl.-Ing. Uwe Stehr (IMST GmbH)

Prof. Dr. - Ing K. Solbach

Chair of Department of High Frequency Technique

University Duisburg - Essen



University of Duisburg-Essen



Wireless Communication


Cellular Telephones

wireless LAN's
GPS/satellite
Receivers

small size

low-cost low power

small form

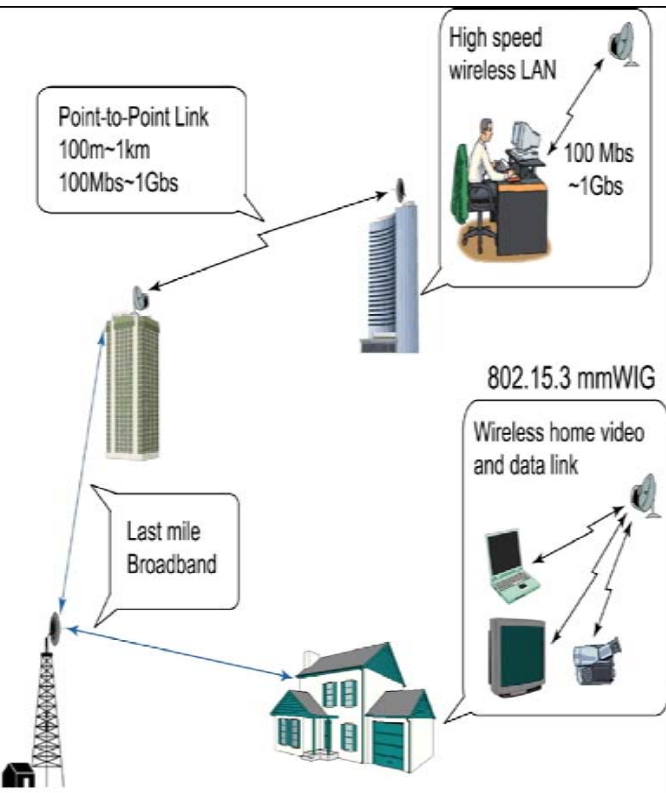



Voltage Controlled Oscillators

- Applications

- *PLL-Based Applications*

- *Non-PLL Based Applications*



Voltage Controlled Oscillators

*Base Station
Cell Phone*

Telecommunication

GPS & Navigation


Satellite Communication

LAN/WAN


Military

■ Applications


VCO in Digital & Analog Applications

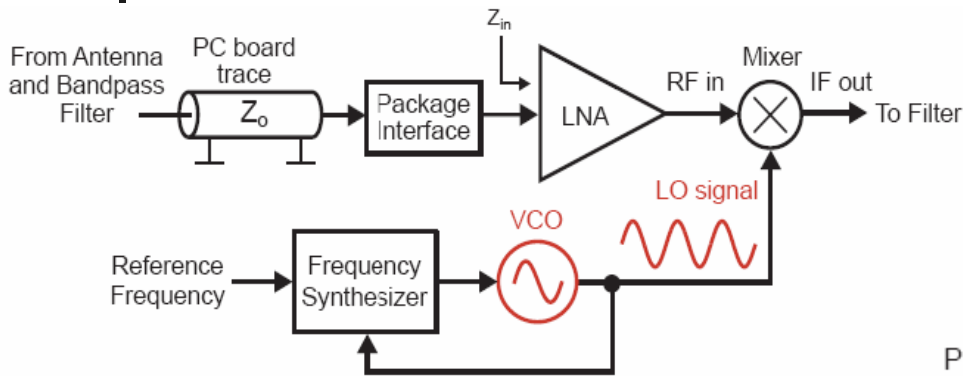

VCO for Analog wireless system

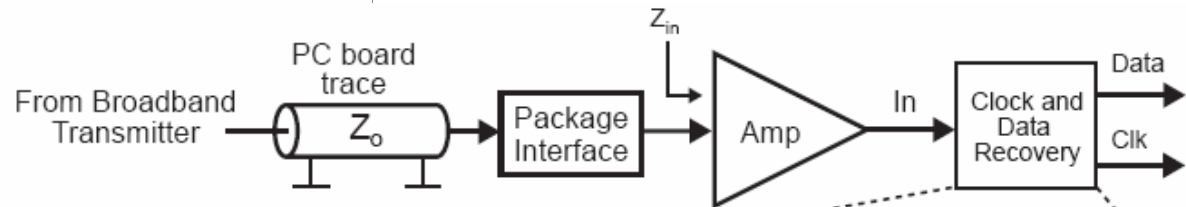

VCO for High speed data link

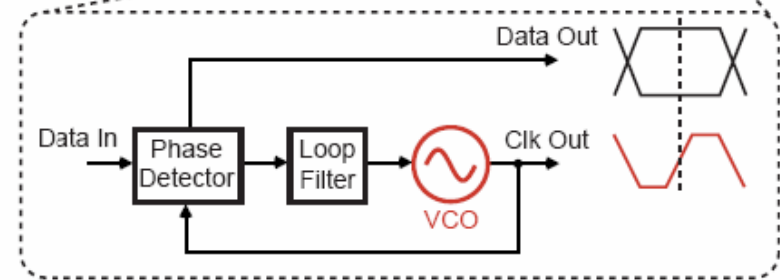



Design Goals


- Design integrated on-chip inductor optimized for low phase noise
- VCO Core
- Stable on-chip power amplifier
- The matching between the core and PA and PA and load



Target Design Specifications


- Frequency 23.9- 24.35 GHz
- Out put Power 6 dBm
- Supply Voltage 3.2V to 3.4V
- Supply Current <50mA
- Phase Noise <-70 dBc/Hz @ 100 KHz offset
- Tuning Voltage Range 0.4 to 2.8 V
- Temperature Range -40° C to 105° C
- Layout < 1 mm^2

Some Theories

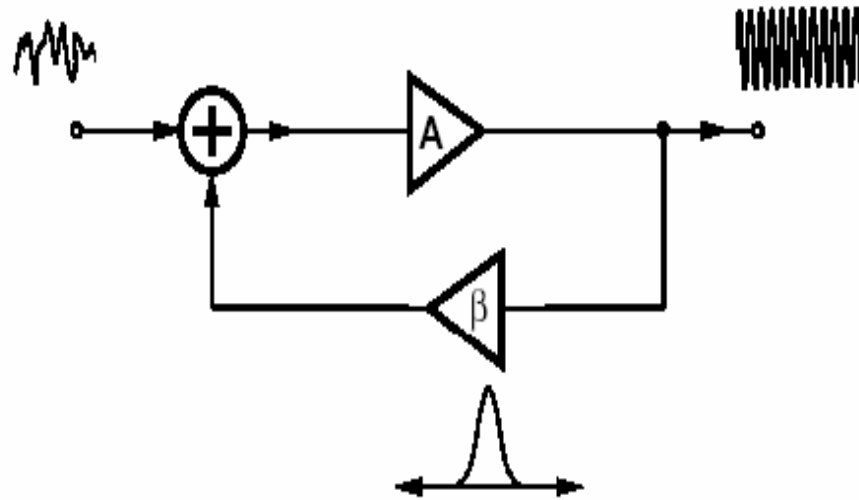

$$H(s) = \frac{A(s)}{1 - A(s) \times \beta(s)}$$

Some Theories

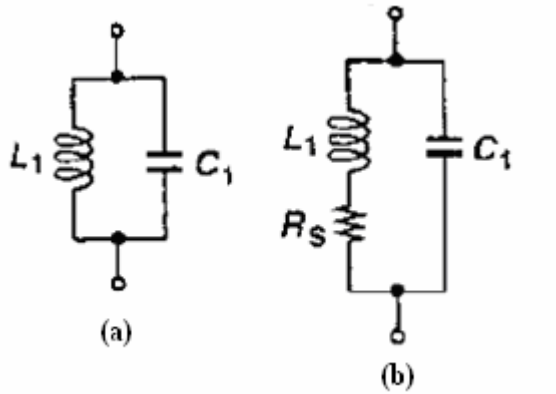


$$\frac{-1}{j\omega C_1}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$j\omega L_1$$

$$Q \rightarrow \infty$$

How about the VCO?

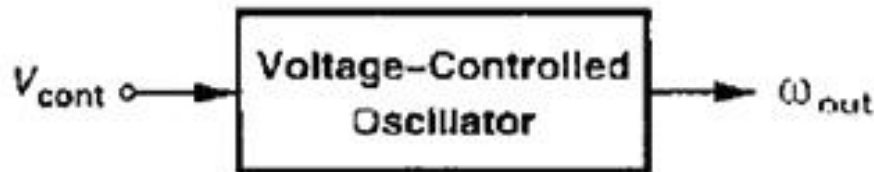

$L \sim 70 \text{ pH}$

$C \sim 0.65 \text{ pF}$


$f \sim 24 \text{ GHz}$

$K_{VCO} \sim 2 \text{ GHz/V}$


$$\omega_{\text{out}} = \omega_0 + K_{VCO} V_{\text{cont}}$$

$V_{\text{cont}} = 0$

VCO gain (rad/sV)

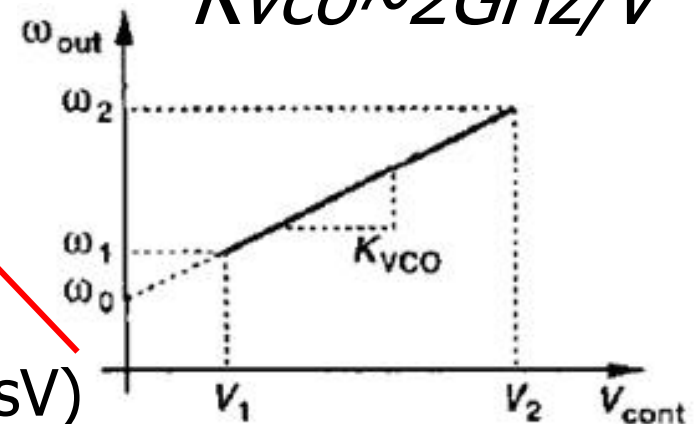


Noise in Oscillators

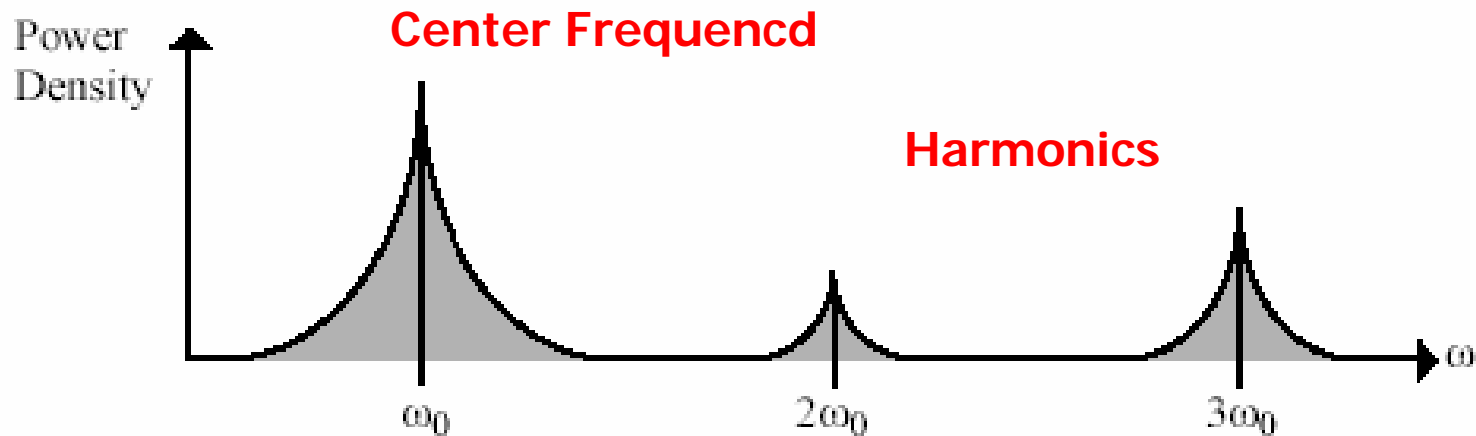


Practical Oscillator Spectrum

Phase Noise

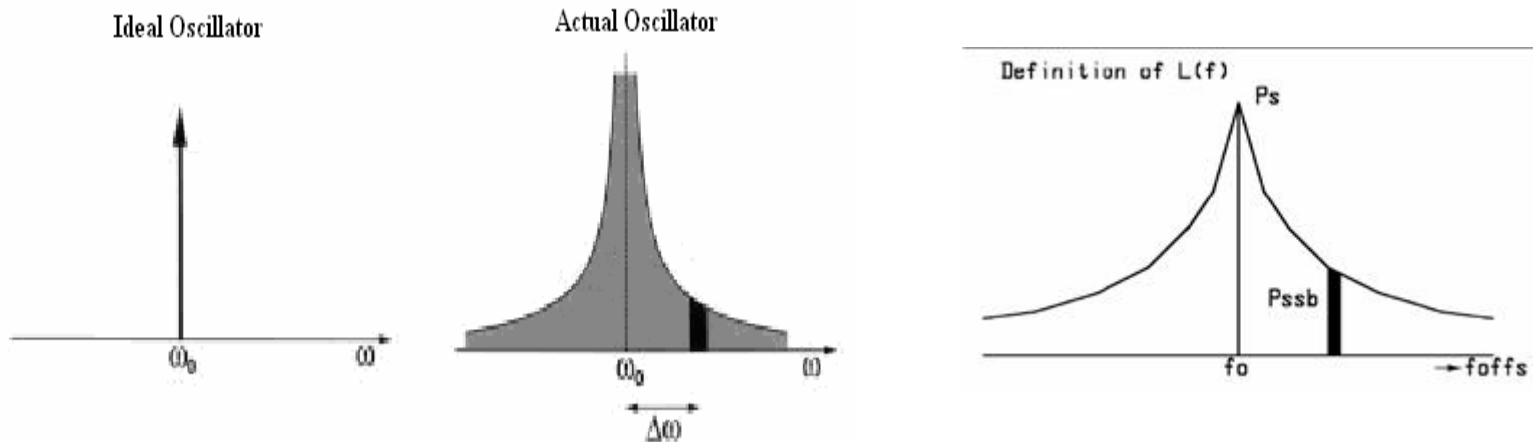

$$L(f) = \frac{P_{ssb} \text{ (per 1 Hz)}}{P_s}$$

Phase Noise

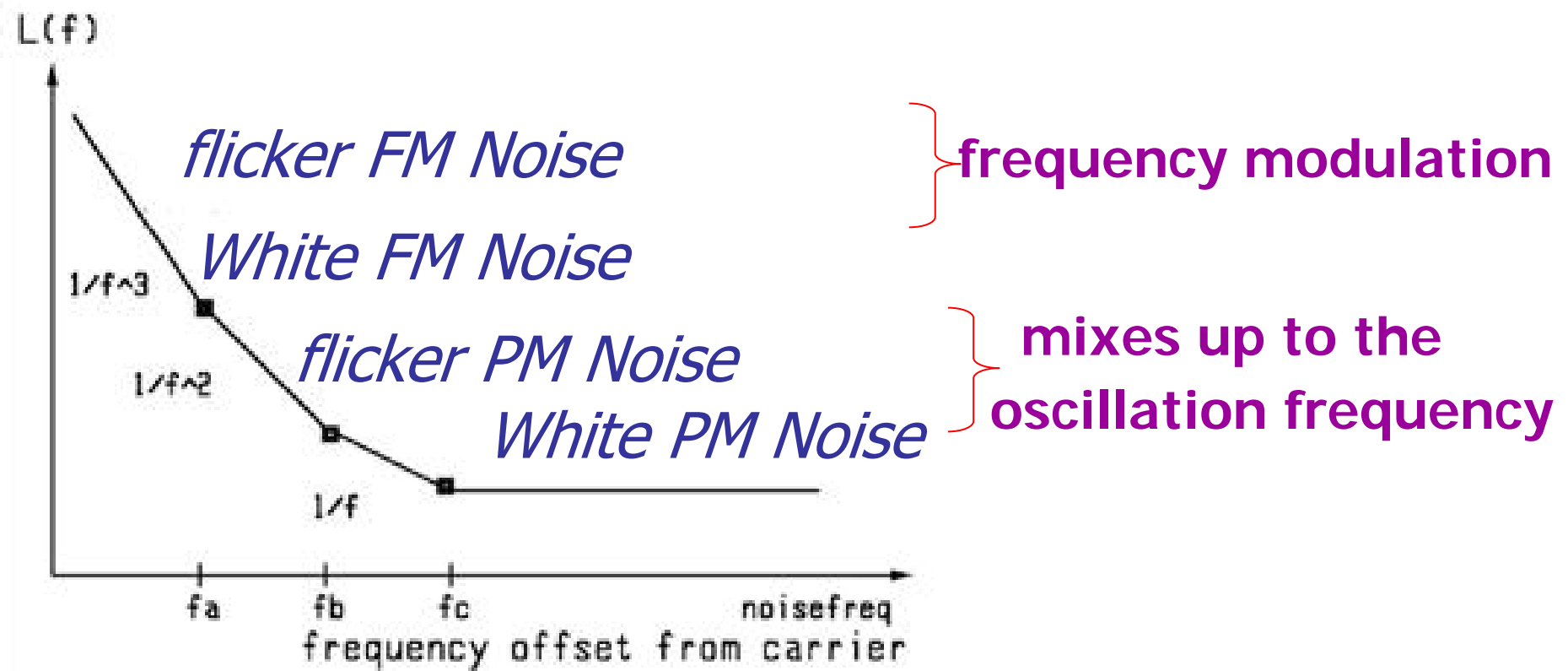



Leeson's Model

$$L\{\Delta\omega\} = \left\{ \frac{2FKT}{P_s} \left[1 + \left(\frac{\omega_0}{2Q\Delta\omega} \right)^2 \right] \left[1 + \frac{\omega \frac{1}{f^3}}{|\Delta\omega|} \right] \right\}$$

■ Q is the quality factor of the tank


■ P_s is the average power dissipated in the tank



How to reduce Phase Noise

- The average power dissipated in the tank resistance
- Quality factor with the Power 2
- Low Noise Power Supply and Tuning Voltage
- Grounding HF and DC
- Connections to the tuning port: short, screened, shielded, decoupled
- Capacitor Bank

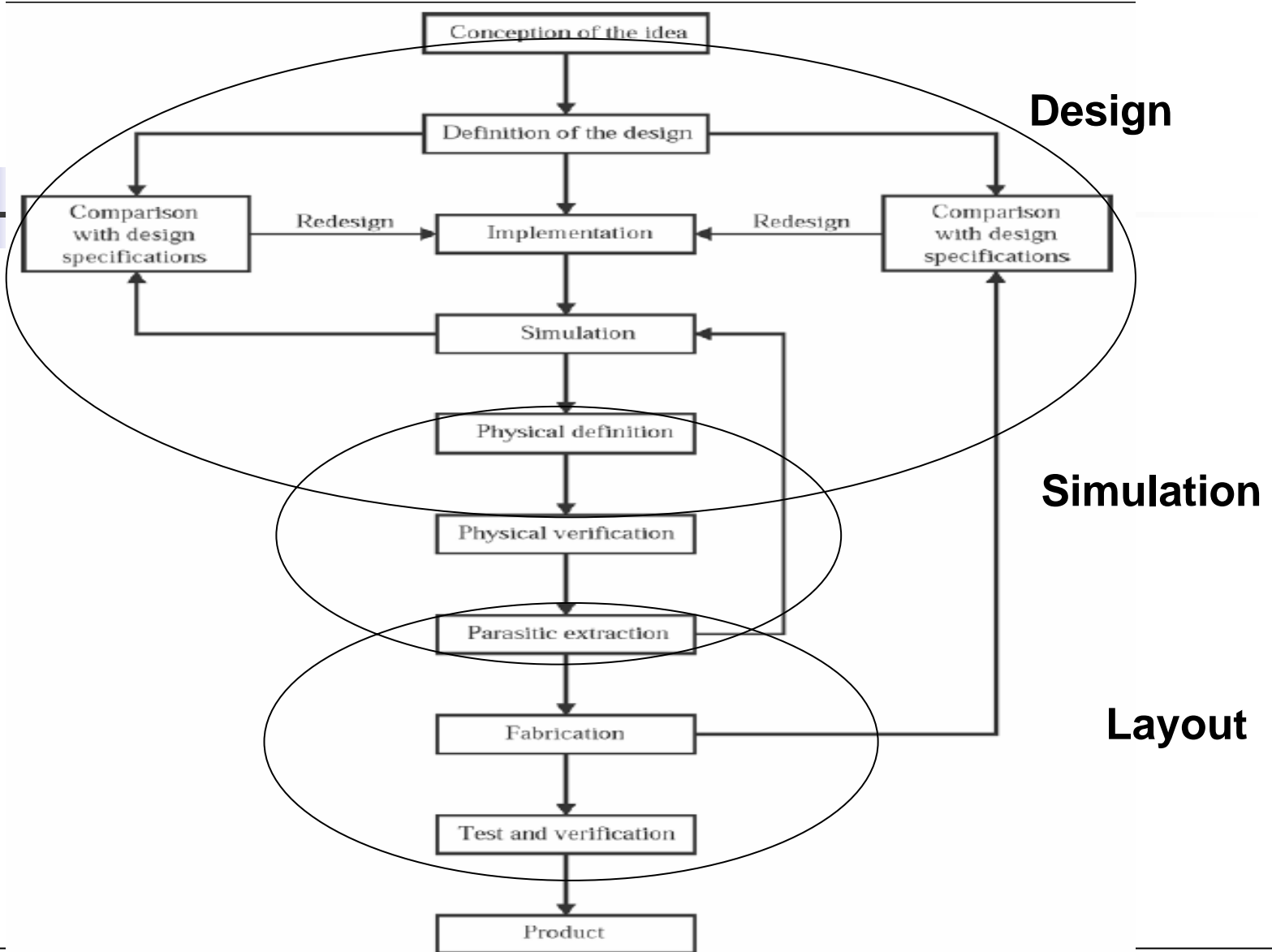Design Process flow for Analog Integrated Circuits





The applied technology

- **B7HF200_8 200 GHz Bipolar technology**
200 GHz SiGe / (silicon-germanium) bipolar process with copper metallization for mixed analogue / digital HF applications


High speed and ultra high speed npn Transistors

Varactors MIM capacitors 3 kind of Resistors

No Inductor

Frequency Operation Point

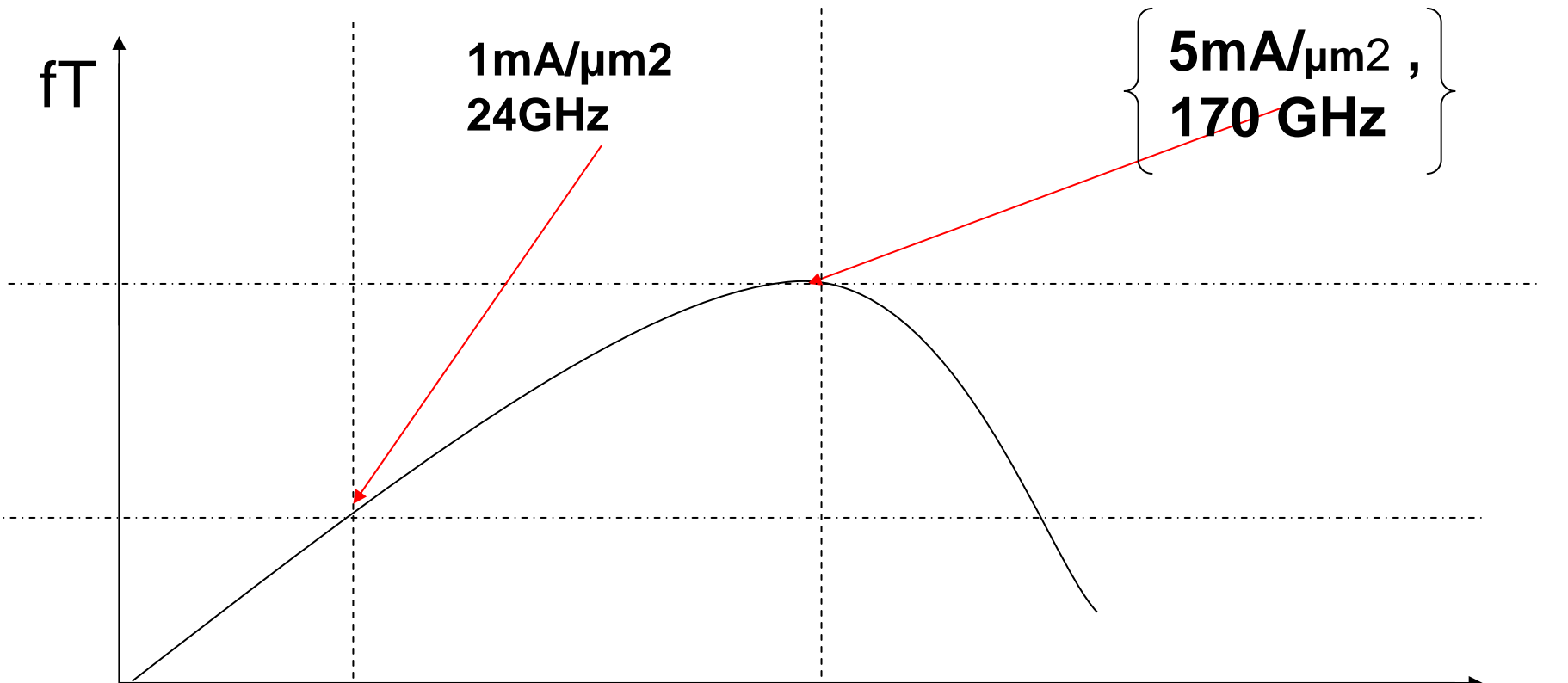f_T (@ $jC = 5 \text{ mA}/\mu\text{m}^2$) = 170 GHz , $V_{(BR)}=1.5-6$





Inductors

On-chip spiral inductors



Very non ideal behaviour

Rather low Q

Size depends on the current







Width < 15 um

Symmetric, Differential L=70pH Q=15

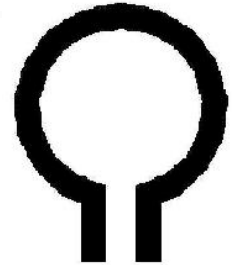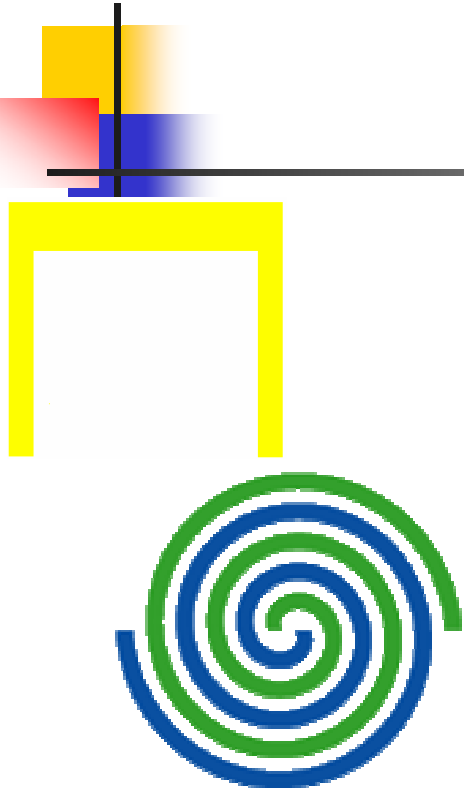



Losses in Integrated Inductors

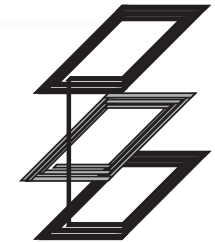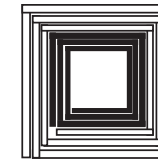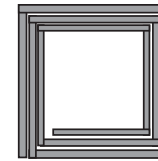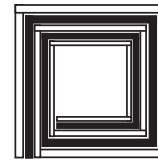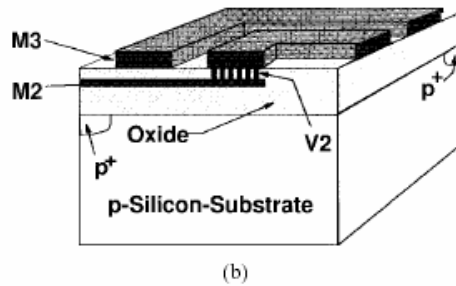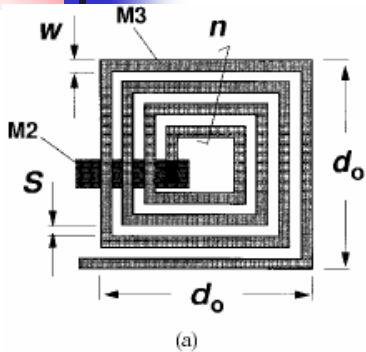

low frequencies,

higher frequencies




metal & via resistance constant

Q proportional to Frequency and affected by the substrate.

Q directly proportional to frequency skin effect

Q is proportional to square root of Frequency.

Greenhouse's Model

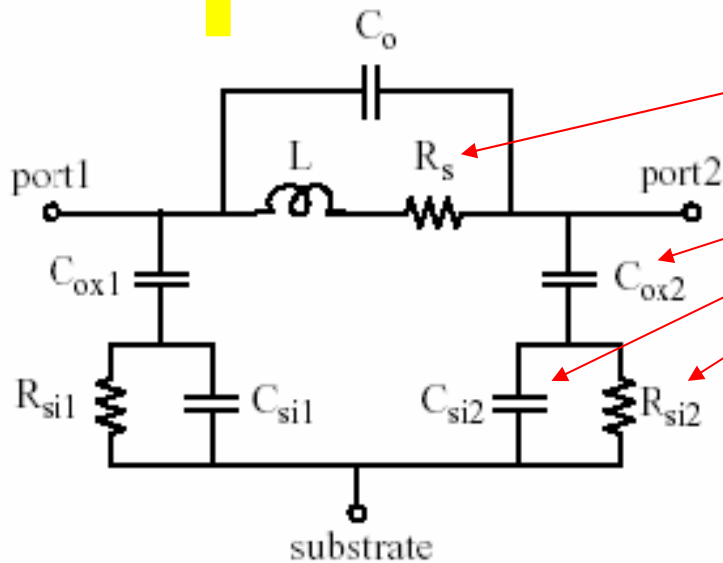 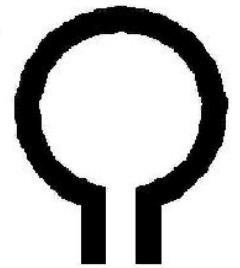


Series resistance of the spiral
between the metal layer and substrate

What affects the resistance of a microstrip line
in a silicon technology?


DC Current, Edge effect, Proximity effect
and Skin effect

cadence™ VCO Core

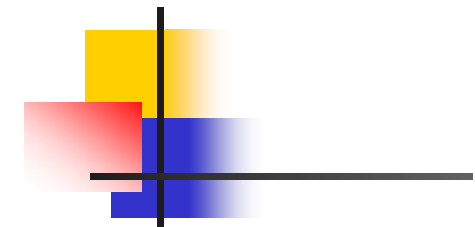

Negative resistance
cross-coupled pairs

Current Source

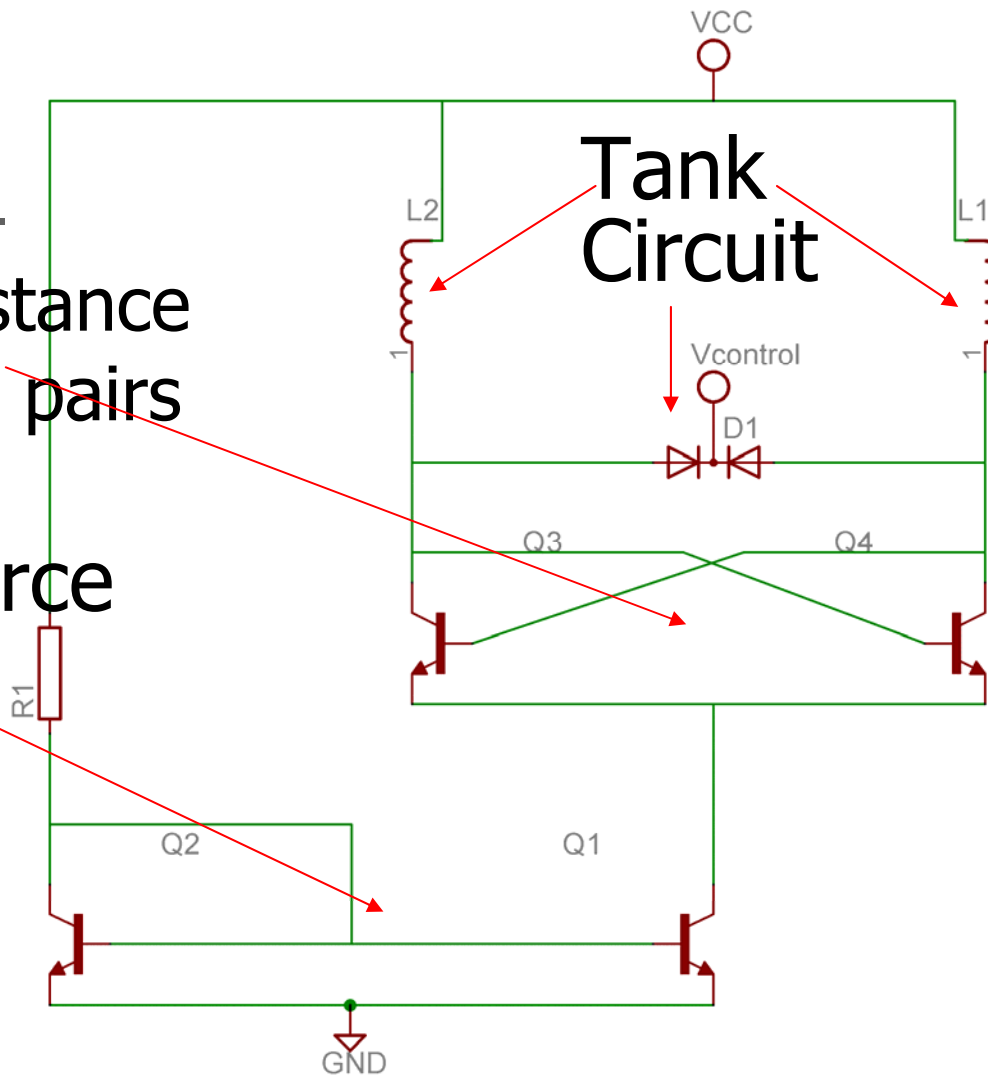




Negative Resistance Circuit

■ Advantages :


- Simple topology
- Good for feeding differential circuits
- Good phase noise performance can be achieved, it can reject common mode noise,
- Has better power supply noise rejection,
- Easier to bias on-chip without any ideal ground available.


Analysis

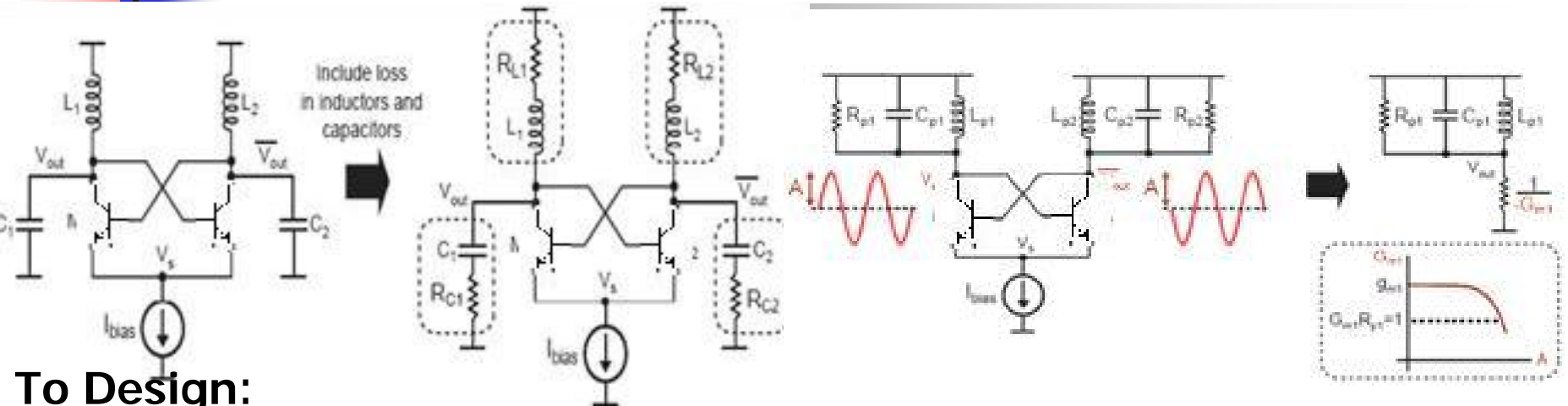


- To Design:**
1. tank components
 2. bias current
 3. transistor size

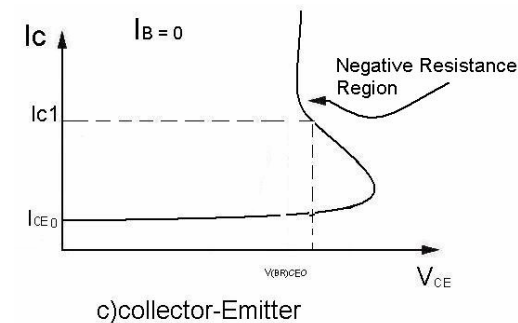Gm is the large signal transconductance value



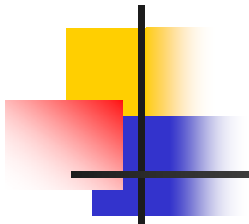


Simulation Results

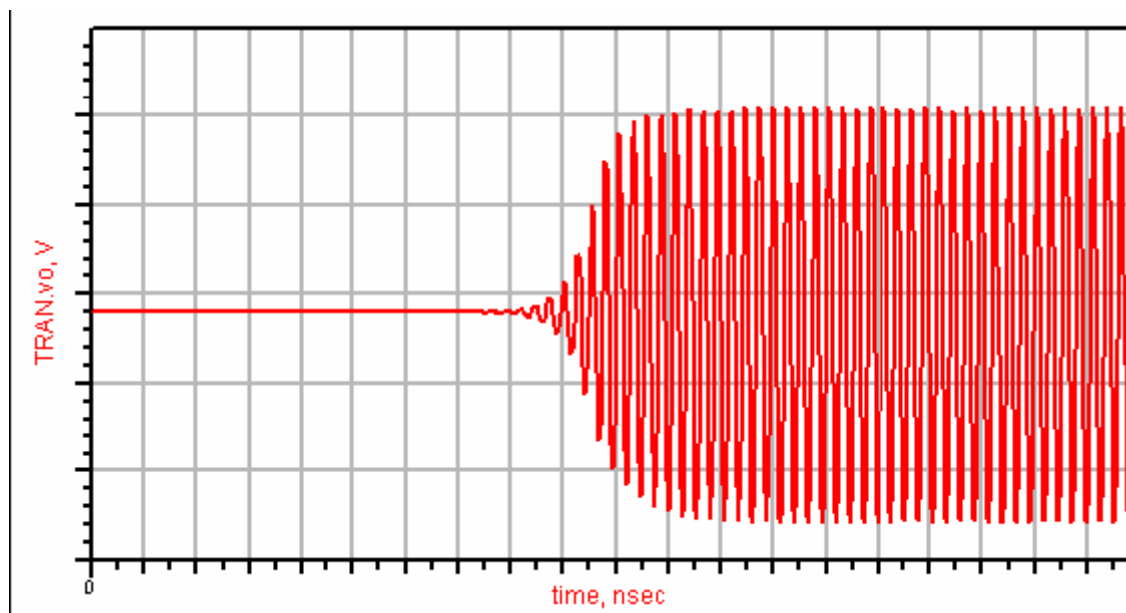

1.8 V p-p

Amplifier

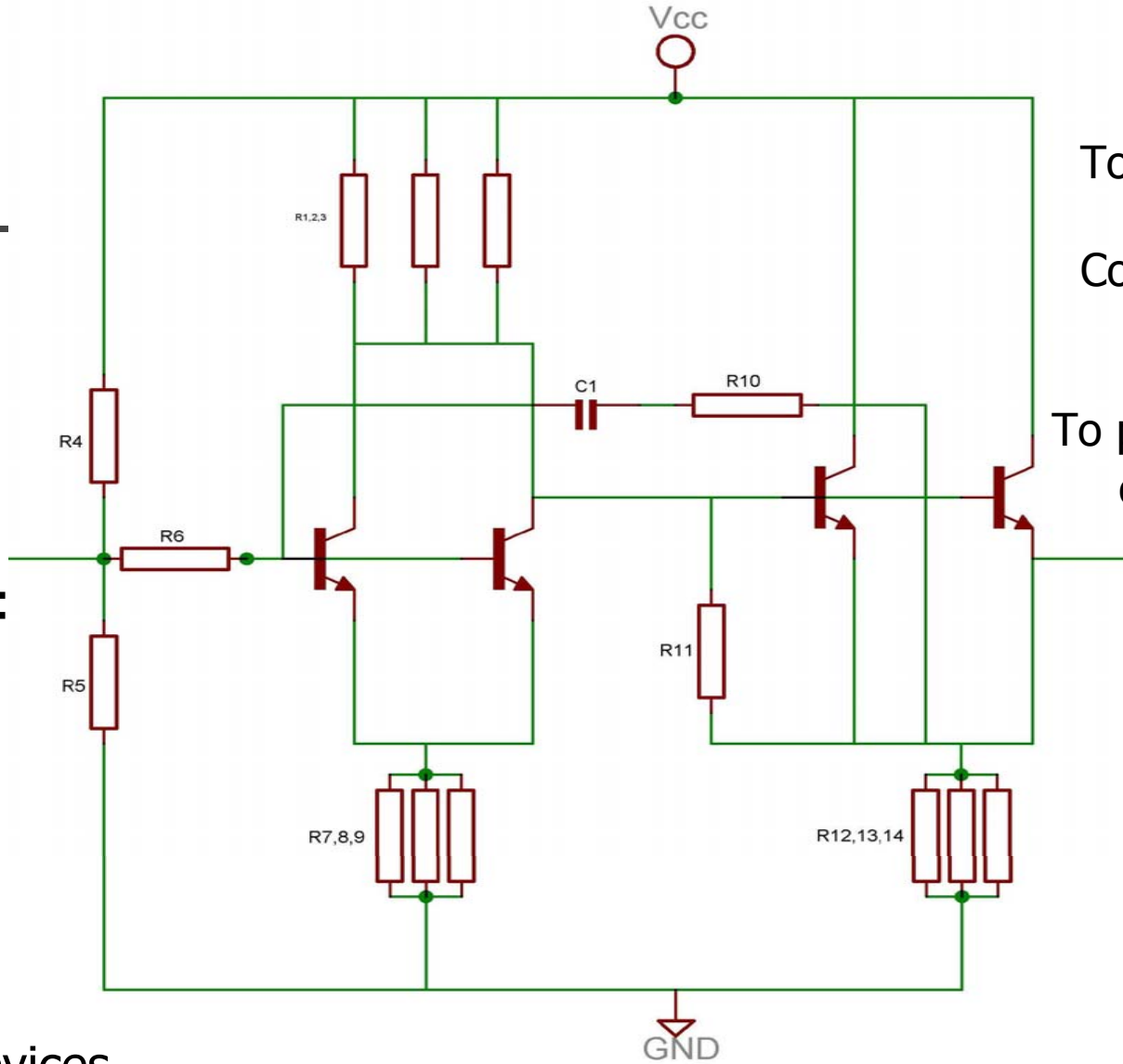

To decouple the
Core & external load

To provide sufficient
output power.

Biasing
in
Class A

Disadvntage:
Conduction
angel

Battery

Active devices

Fourier analysis of the Current wave form

$$I_n = \int_{-\alpha/2}^{\alpha/2} \frac{I_{\max}}{1 - \cos(\frac{\alpha}{2})} \left[\cos(\theta) - \cos(\frac{\alpha}{2}) \right] \cos(n\theta) d\theta$$

$$I_{dc} = \frac{I_{\max}}{2\pi} \frac{2 \sin(\frac{\alpha}{2}) - \alpha \cos(\frac{\alpha}{2})}{1 - \cos(\frac{\alpha}{2})}$$

$$P_{dc} = V_{dc} \times I_{dc} \quad P_1 = \frac{V_{dc}}{\sqrt{2}} \frac{I_1}{\sqrt{2}}$$


**20Log V = 6dBm ,
V=0.44**

**Ac denn 0.44 * 1.4 =
0.63 v Amplitude**

**10Log(P) = 6dBm
p=4mW**

P=R*I^2 I=9mA

Stability Calculations

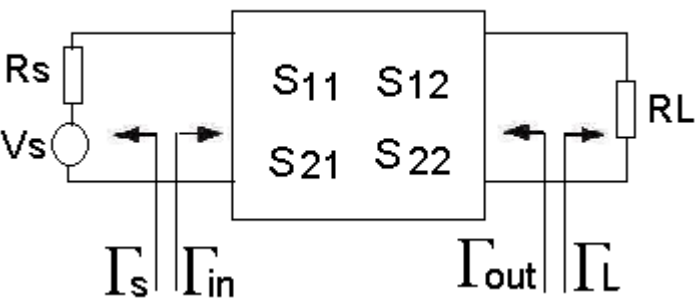

The circuit is Unconditionally Stable if

$$\text{and } \begin{cases} |\Gamma_{in}| < 1 \\ |\Gamma_{out}| < 1 \end{cases}$$

for all values of R_s and R_L

$$K = \frac{1 - |S_{11}|^2 - |S_{22}|^2 + |\Delta|^2}{2 |S_{12}S_{21}|} > 1$$

$$\Delta = S_{11}S_{22} - S_{12}S_{21}$$



Stability Circles

- Drawing the locus of the source and load terminations on the Smith Chart

for Source stability Circle $|\Gamma_{out}| = 1$

$$r_s = \frac{|S_{12}S_{21}|}{S_{11}^2 - \Delta^2} \quad C_s = \frac{(S_{11}\Delta S_{22}^*)^*}{S_{11}^2 - \Delta^2} = |C_s| \angle \theta$$

for Load stability Circle $|\Gamma_{in}| = 1$

$$r_L = \frac{|S_{12}S_{21}|}{S_{22}^2 - \Delta^2} \quad C_L = \frac{(S_{22}\Delta S_{11}^*)^*}{S_{22}^2 - \Delta^2} = |C_L| \angle \theta$$

Stability Circles

$$r_L = \frac{|S_{12}S_{21}|}{S_{22}^2 - \Delta^2}$$


$$C_L = \frac{(S_{22}\Delta S_{11}^*)^*}{S_{22}^2 - \Delta^2} = |C_L| \angle \theta$$

$$r_s = \frac{|S_{12}S_{21}|}{S_{11}^2 - \Delta^2}$$

$$C_s = \frac{(S_{11}\Delta S_{22}^*)^*}{S_{11}^2 - \Delta^2} = |C_s| \angle \theta$$


Source Stability Circle

$$|\Gamma_{out}| = 1$$

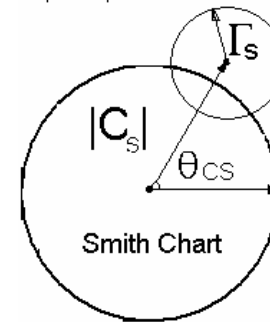

Load Stability Circle

$$|\Gamma_{in}| = 1$$

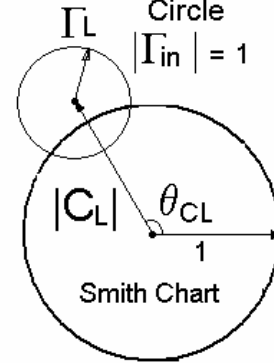

Load stability
Circle

$$S_{22} > 1$$

The area including the centre is **unstable**

$$S_{22} < 1$$

The area including the center is **stable**

Source stability
Circle

$$S_{11} > 1$$




The area including the centre is **unstable**

$$S_{11} < 1$$

The area including the centre is **stable**


How to make an Amplifier Stable?

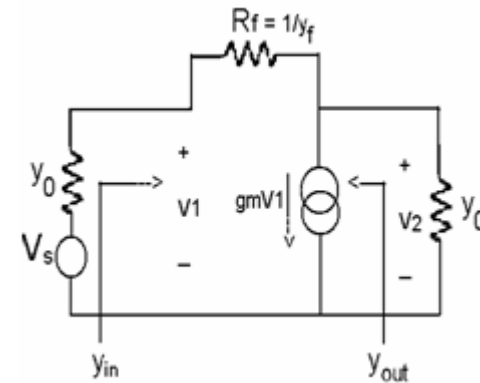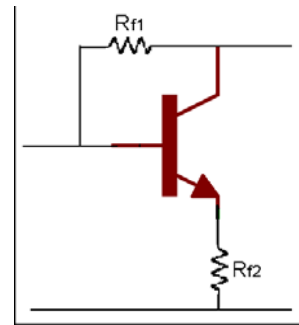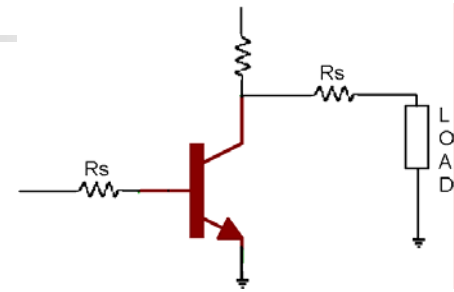- Add a resistor(Seri or Parallel)
- Feed back Amplifier




$$y_f = \frac{y_0}{1 + |S_{21}|} \quad \text{or} \quad R_f = R_0(1 + |S_{21}|)$$

The Complete Circuit

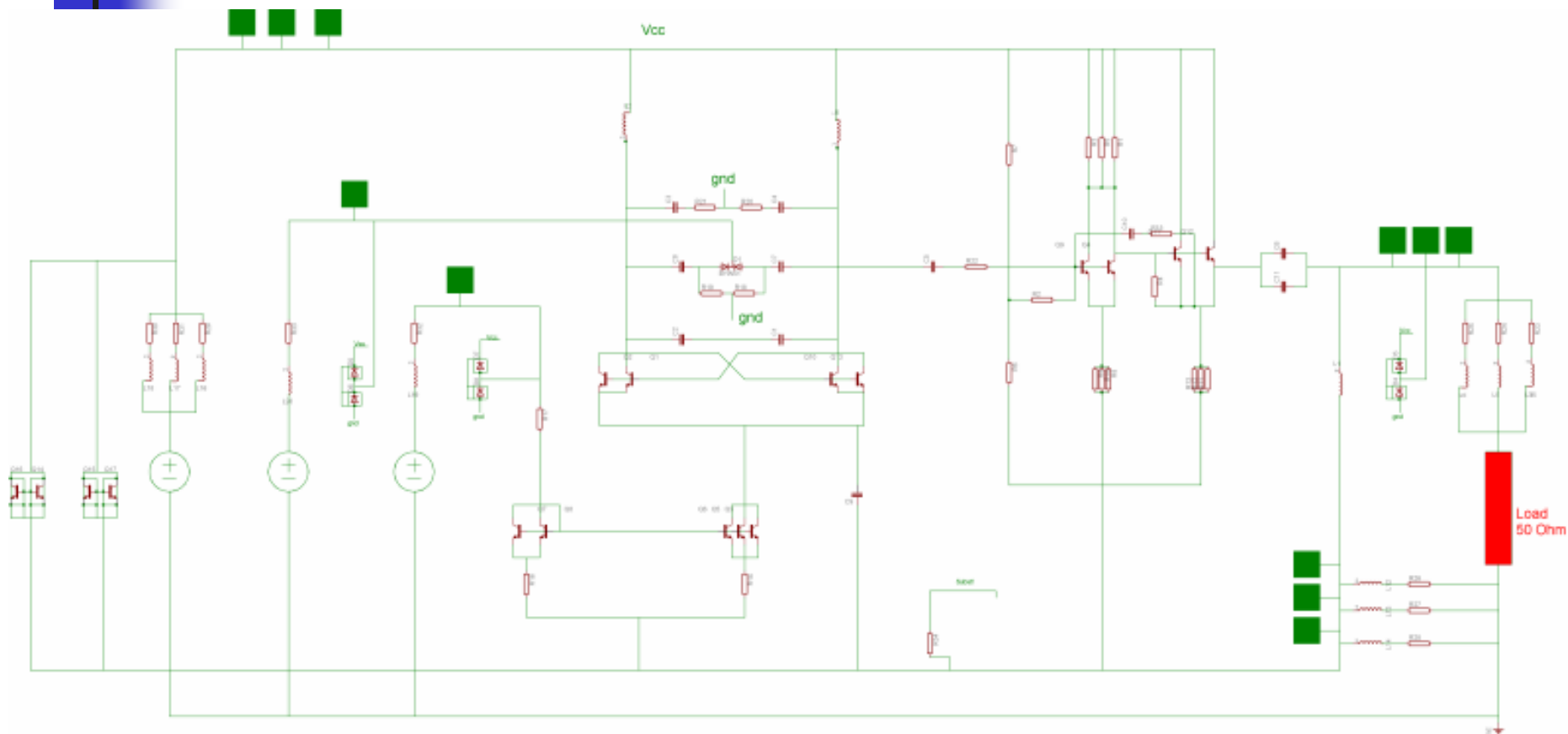


Simulation Results

Transient Response

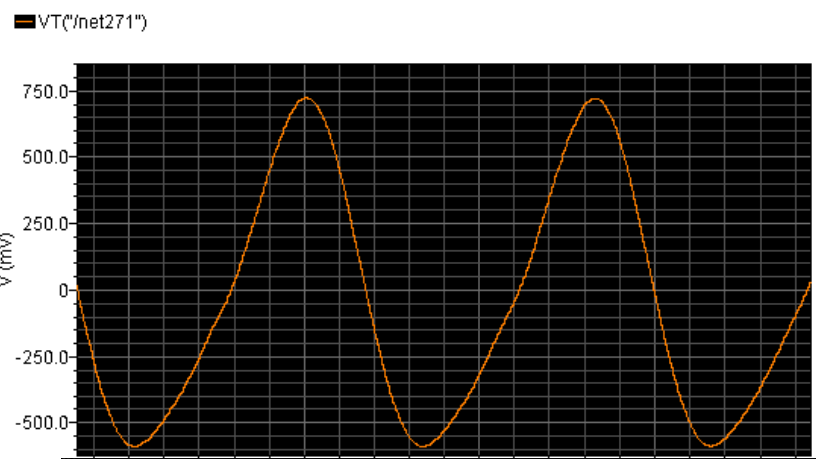

Spectrum

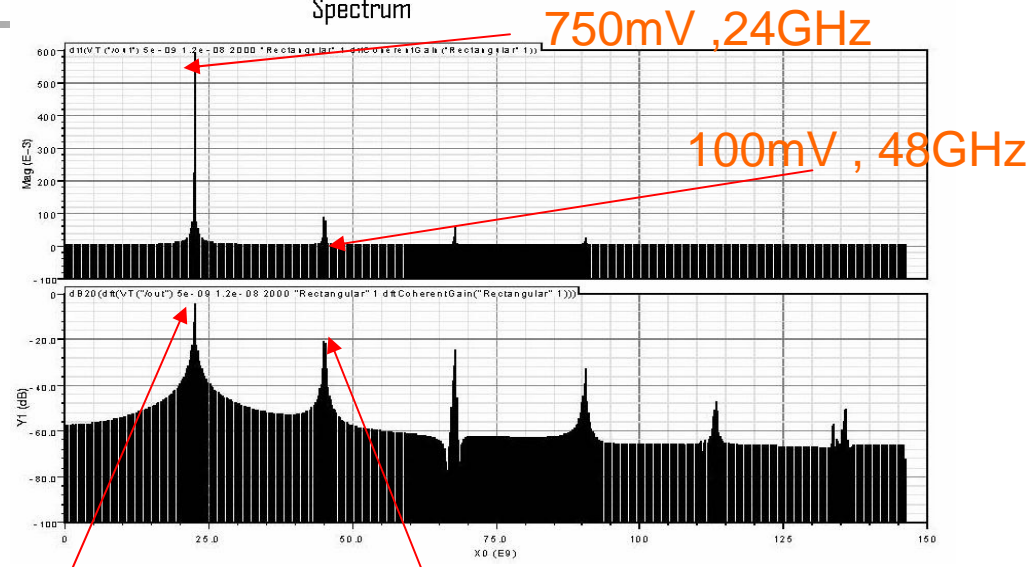





-4dB

-19dB



-75dBc/hz @ 100KHz



Simulation Results

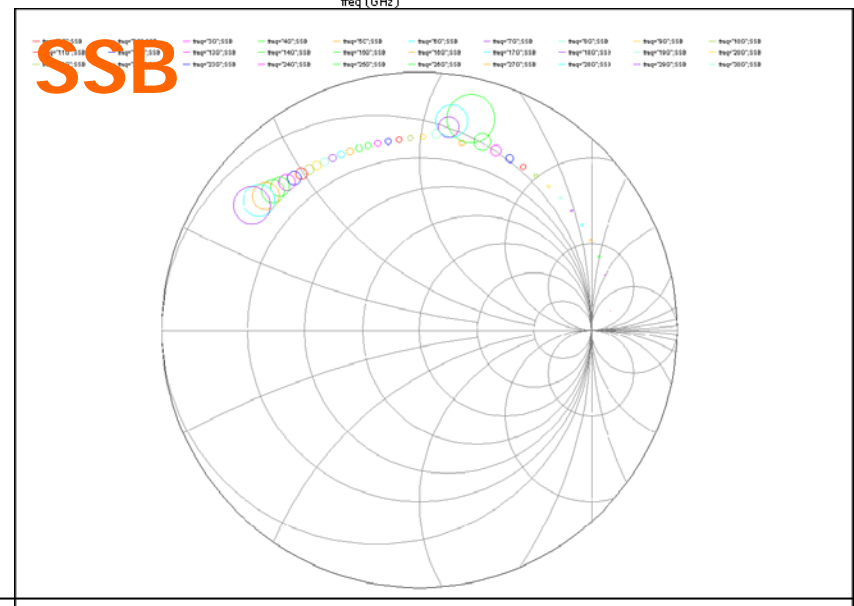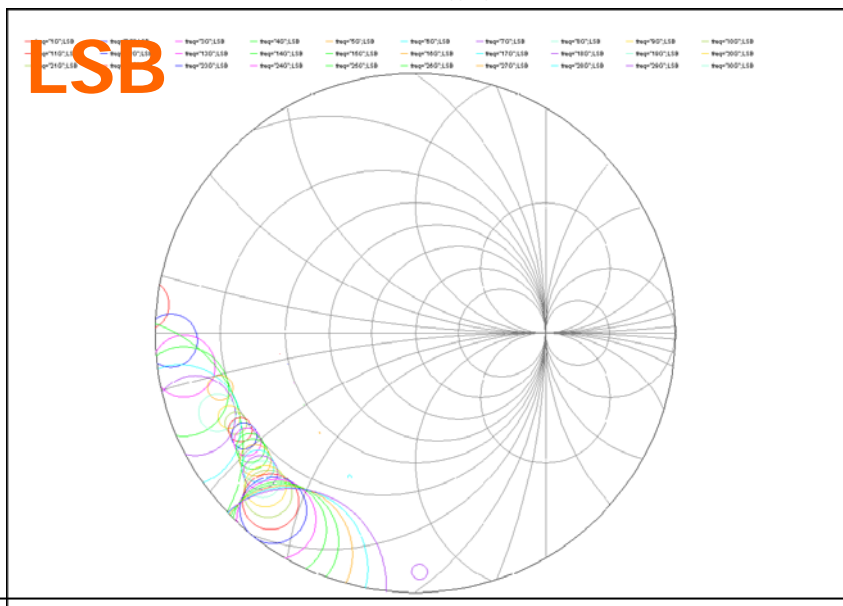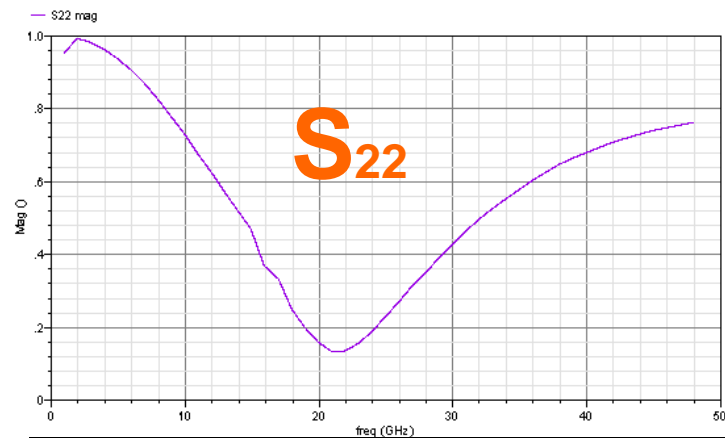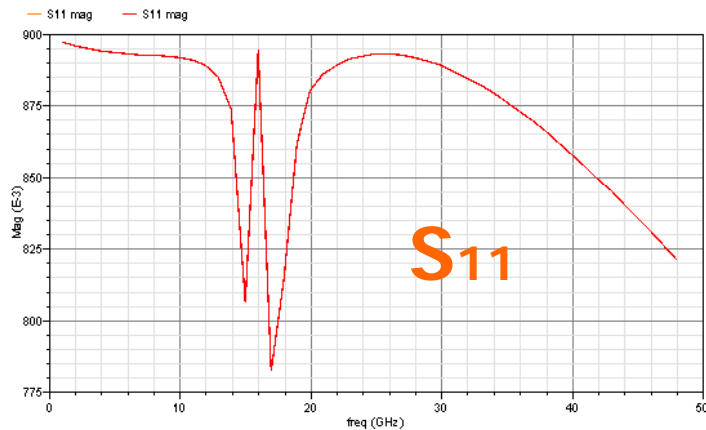


Layout

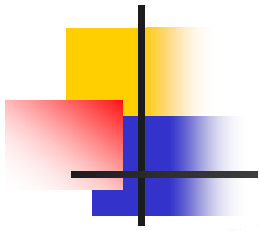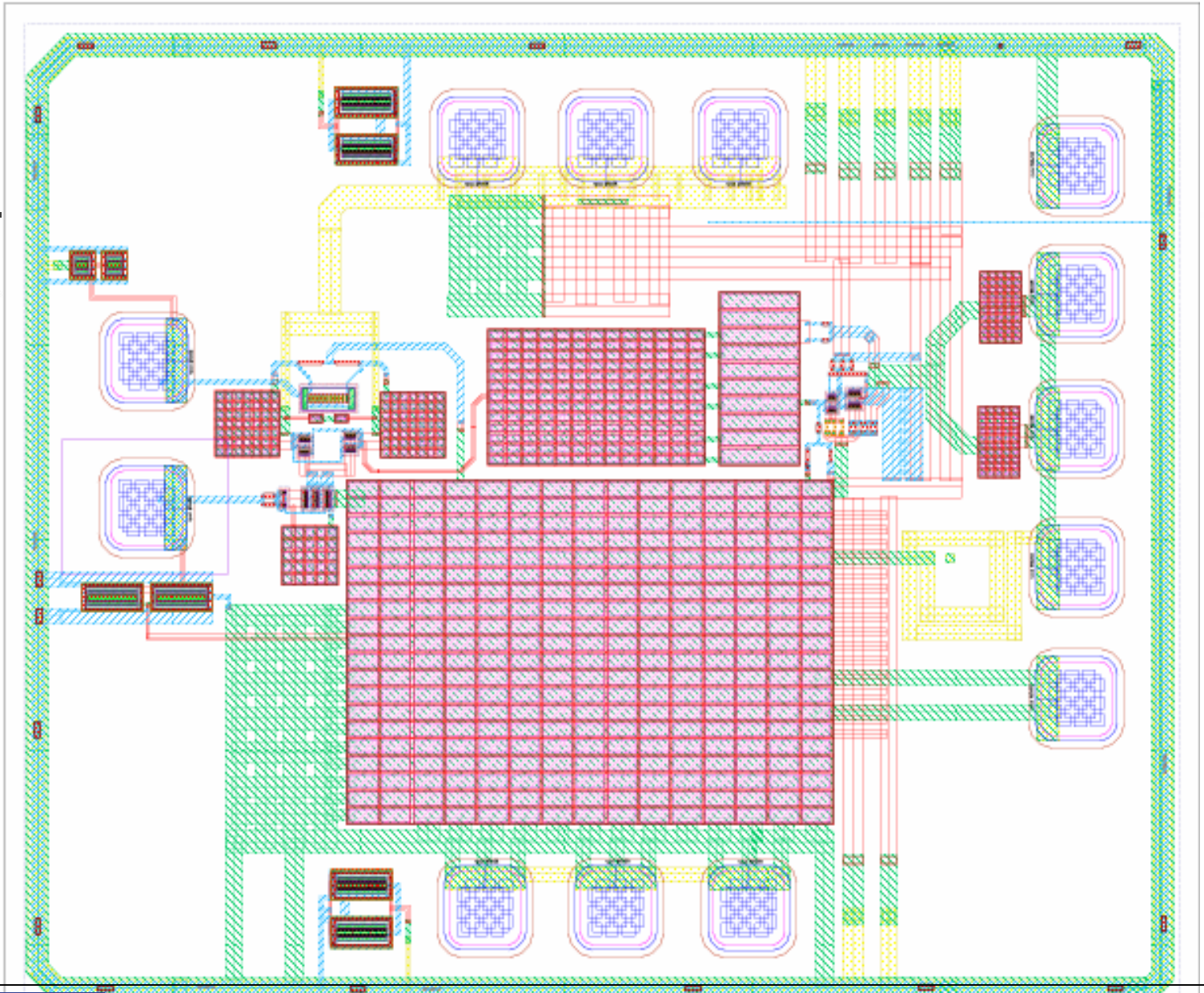

0.7 mm^2

Symmetric

Parasitics
Extraction

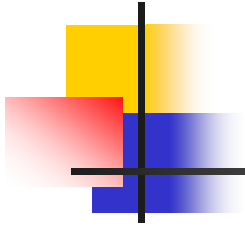

Thanks for the attention